
 


Sequential Logic Design


Bit Storage Summary

 


Feature: $S=1$ sets Q to 1, $R=1$ resets Q to 0. Problem: $SR=11$ yield undefined Q .



 Feature: S and R only have effect when $C=1$. We can design outside circuit so $SR=11$ never happens when $C=1$. Problem: avoiding $SR=11$ can be a burden.



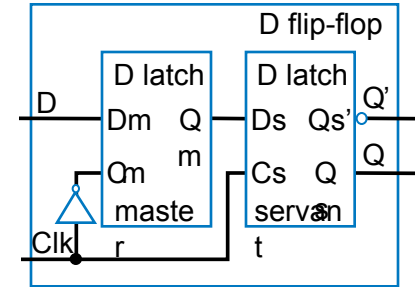Feature: SR can't be 11 if D is stable before and while $C=1$, and will be 11 for only a brief glitch even if D changes while $C=1$. Problem: $C=1$ too long propagates new values through too many latches: too short may not enable a store.



Feature: Only loads D value present at rising clock edge, so values can't propagate to other flip-flops during same clock cycle. Tradeoff: uses more gates internally than D latch, and requires more external gates than SR – but gate count is less of an issue today.


- We considered increasingly better bit storage until we arrived at the robust D flip-flop bit storage

State Diagrams for Various Flip-Flops


NAME

STATE DIAGRAM


SR

 


JK




 


D

 


T

 


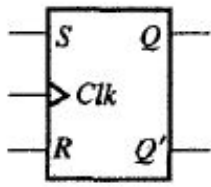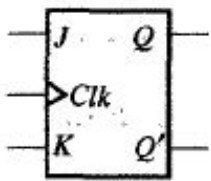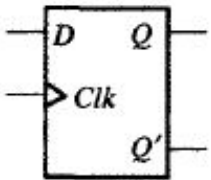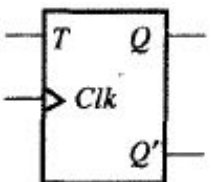FLIP-FLOP NAME	FLIP-FLOP SYMBOL	CHARACTERISTIC TABLE	CHARACTERISTIC EQUATION	EXCITATION TABLE																																			
SR		<table><tr><th>S</th><th>R</th><th>Q(next)</th></tr><tr><td>0</td><td>0</td><td>Q</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>NA</td></tr></table>	S	R	Q(next)	0	0	Q	0	1	0	1	0	1	1	1	NA	$Q(next) = S + R'Q$ $SR = 0$	<table><tr><th>Q</th><th>Q(next)</th><th>S</th><th>R</th></tr><tr><td>0</td><td>0</td><td>0</td><td>X</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>X</td><td>0</td></tr></table>	Q	Q(next)	S	R	0	0	0	X	0	1	1	0	1	0	0	1	1	1	X	0
S	R	Q(next)																																					
0	0	Q																																					
0	1	0																																					
1	0	1																																					
1	1	NA																																					
Q	Q(next)	S	R																																				
0	0	0	X																																				
0	1	1	0																																				
1	0	0	1																																				
1	1	X	0																																				
JK		<table><tr><th>J</th><th>K</th><th>Q(next)</th></tr><tr><td>0</td><td>0</td><td>Q</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>Q'</td></tr></table>	J	K	Q(next)	0	0	Q	0	1	0	1	0	1	1	1	Q'	$Q(next) = JQ' + K'Q$	<table><tr><th>Q</th><th>Q(next)</th><th>J</th><th>K</th></tr><tr><td>0</td><td>0</td><td>0</td><td>X</td></tr><tr><td>0</td><td>1</td><td>1</td><td>X</td></tr><tr><td>1</td><td>0</td><td>X</td><td>1</td></tr><tr><td>1</td><td>1</td><td>X</td><td>0</td></tr></table>	Q	Q(next)	J	K	0	0	0	X	0	1	1	X	1	0	X	1	1	1	X	0
J	K	Q(next)																																					
0	0	Q																																					
0	1	0																																					
1	0	1																																					
1	1	Q'																																					
Q	Q(next)	J	K																																				
0	0	0	X																																				
0	1	1	X																																				
1	0	X	1																																				
1	1	X	0																																				
D		<table><tr><th>D</th><th>Q(next)</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	D	Q(next)	0	0	1	1	$Q(next) = D$	<table><tr><th>Q</th><th>Q(next)</th><th>D</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	Q	Q(next)	D	0	0	0	0	1	1	1	0	0	1	1	1														
D	Q(next)																																						
0	0																																						
1	1																																						
Q	Q(next)	D																																					
0	0	0																																					
0	1	1																																					
1	0	0																																					
1	1	1																																					
T		<table><tr><th>T</th><th>Q(next)</th></tr><tr><td>0</td><td>Q</td></tr><tr><td>1</td><td>Q'</td></tr></table>	T	Q(next)	0	Q	1	Q'	$Q(next) = TQ' + T'Q$	<table><tr><th>Q</th><th>Q(next)</th><th>T</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	Q	Q(next)	T	0	0	0	0	1	1	1	0	1	1	1	0														
T	Q(next)																																						
0	Q																																						
1	Q'																																						
Q	Q(next)	T																																					
0	0	0																																					
0	1	1																																					
1	0	1																																					
1	1	0																																					

Preset and Clear

 


Clocks

 

- **Clock period:** time interval between pulses
 - Above signal: period = 20 ns
- **Clock cycle:** one such time interval
 - Above signal shows 3.5 clock cycles
- **Clock frequency:** $1/\text{period}$
 - Above signal: frequency = $1 / 20 \text{ ns} = 50 \text{ MHz}$
 - $1 \text{ Hz} = 1/\text{s}$


Fre	Perio
100 GHz	0.01 ns
1 GHz	0.1 ns
1 MHz	1 ns
100 MHz	10 ns
10 kHz	100 ns

Clock Generation-Ring Oscillator

 

(a) Ring oscillator

1ns delay for inverter

 



(b) Timing waveform

$$\text{Frequency} = 1/2 * n * t_d$$

$$\text{Frequency} = 1/2 * 5 * 1\text{n} = 100\text{Mhz}$$

Basic Register

  - Typically, we store multi-bit items
 - e.g., storing a 4-bit binary number
- **Register**: multiple flip-flops sharing clock signal
 - From this point, we'll use registers for bit storage
 - No need to think of latches or flip-flops
 - But now you know what's inside a register




Shift Registers

- Shift registers
- Parallel/serial format conversion
 - SISO (serial in serial out)
 - SIPO (serial in parallel out)
 - PISO (parallel in serial out)
 - PIPO (parallel in parallel out)

Shift Register

 - Shift right
 - Move each bit one position right
 - Shift in 0 to leftmost bit




Q: Do four right shifts on 1001, showing value after each shift


A:

1	001 (original)
0	100
00	10
000	1
0000	

 
- Implementation: Connect flip-flop output to next flip-flop's input



Shift Registers

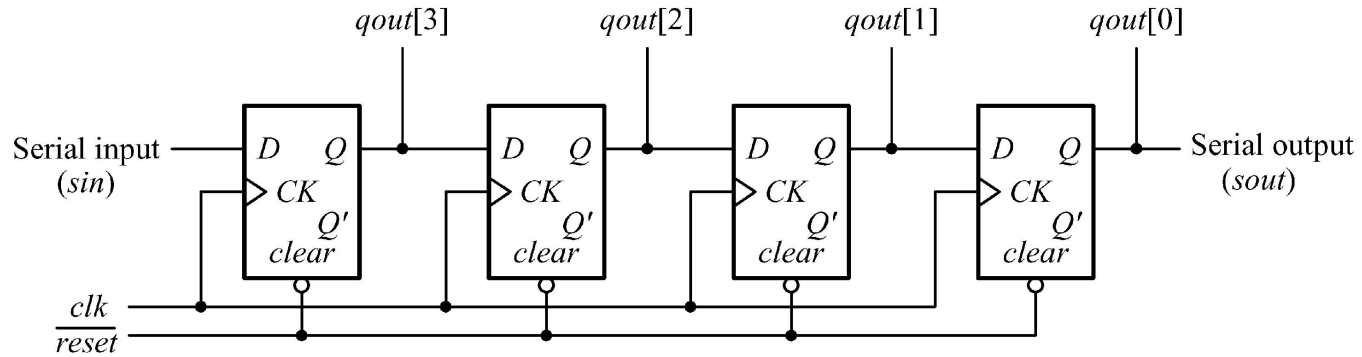


(a) Logic circuit

 

(b) Timing

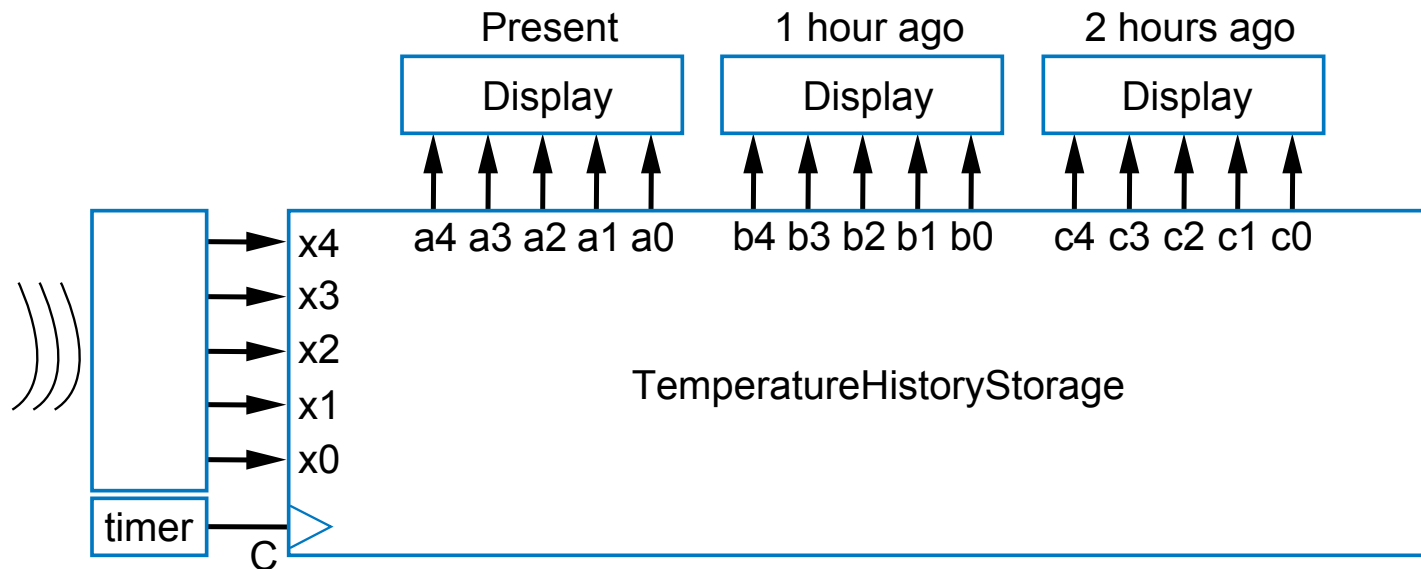
Example Using Registers: Temperature Display

- Temperature history display
 - Sensor outputs temperature as 5-bit binary number
 - Timer pulses C every hour
 - Record temperature on each pulse, display last three recorded values




Register with Parallel Load

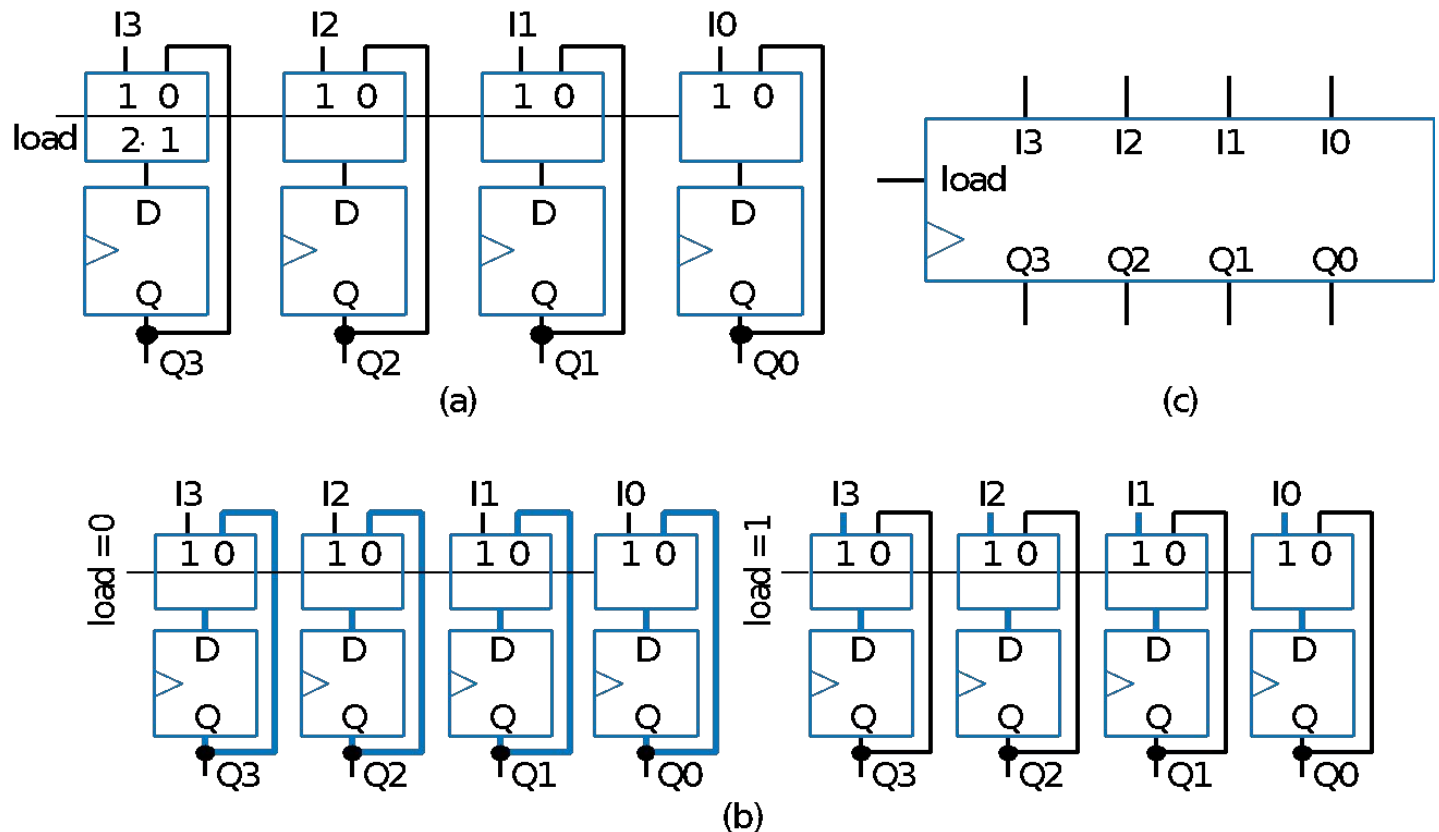- Add 2x1 mux to front of each flip-flop
- Register's load input selects mux input to pass
 - Either existing flip-flop value, or new value to load





Basic Example Using Registers

 - This example will show how registers load simultaneously on clock cycles
 - Notice that all load inputs set to 1 in this example -- just for demonstration purposes




Basic Example Using Registers

 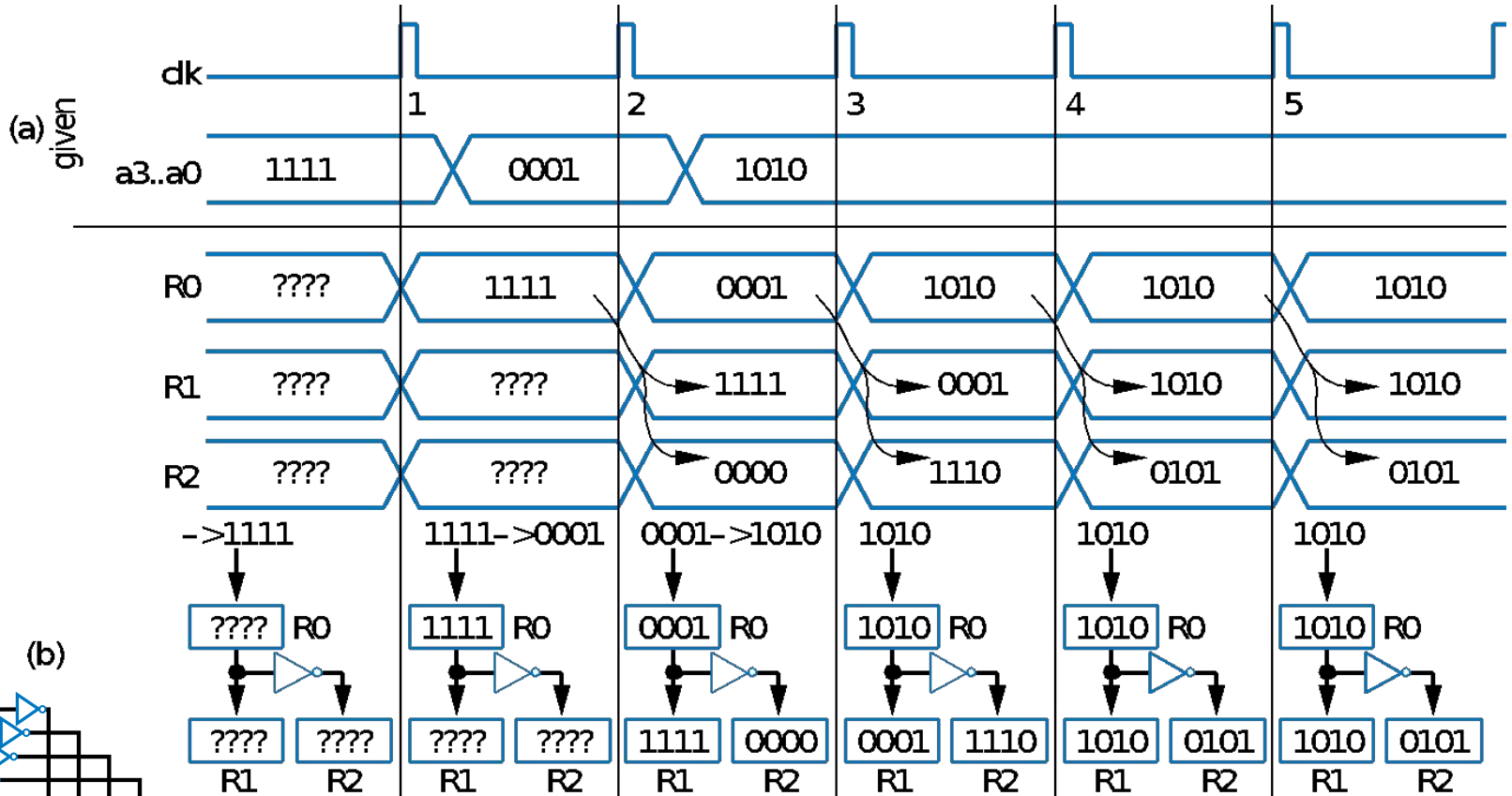

Register Example using the Load Input:

Weight Sampler

 
- Scale has two displays
 - Present weight
 - Saved weight
 - Useful to compare present item with previous item
- Use register to store weight
 - Pressing button causes present weight to be stored in register
 - Register contents always displayed as “Saved weight,” even when new present weight appears



a



Register Example: Temperature History Display

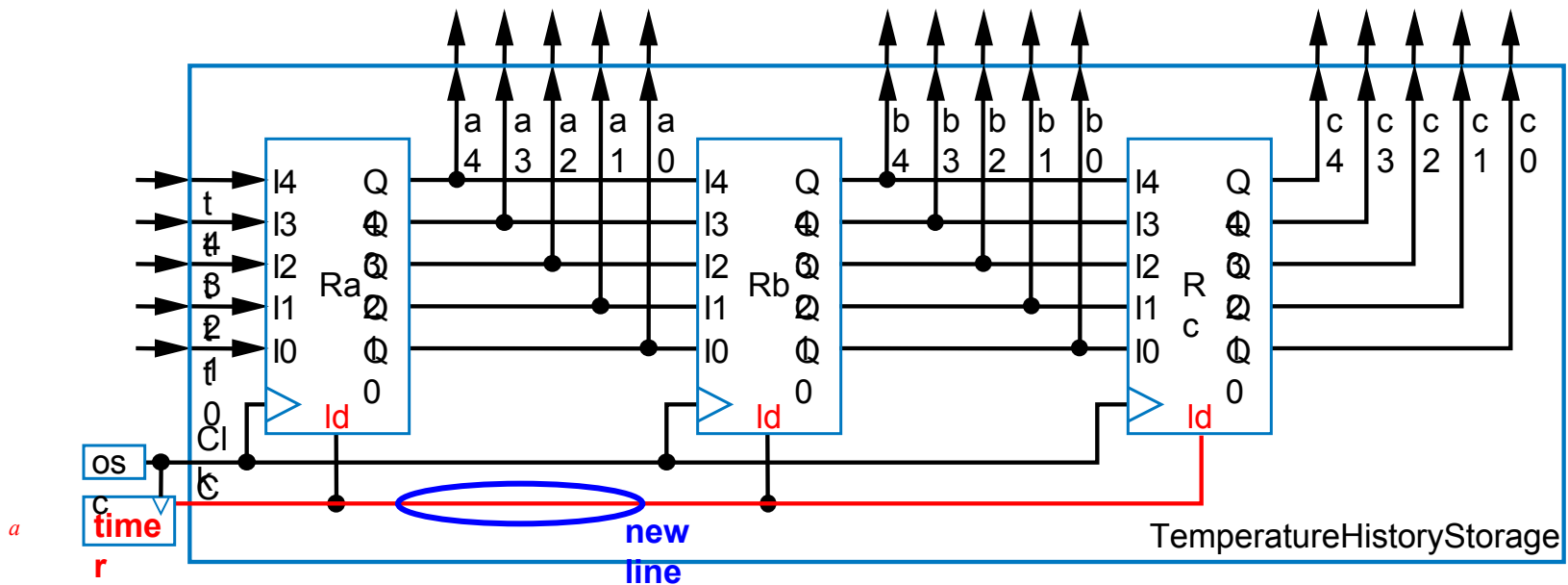- example
 - Timer pulse every hour
 - Previously used as clock. Better design only connects oscillator to clock inputs -- use registers with load input, connect to timer pulse.




Example Using Registers: Temperature Display

- Use three 5-bit registers

 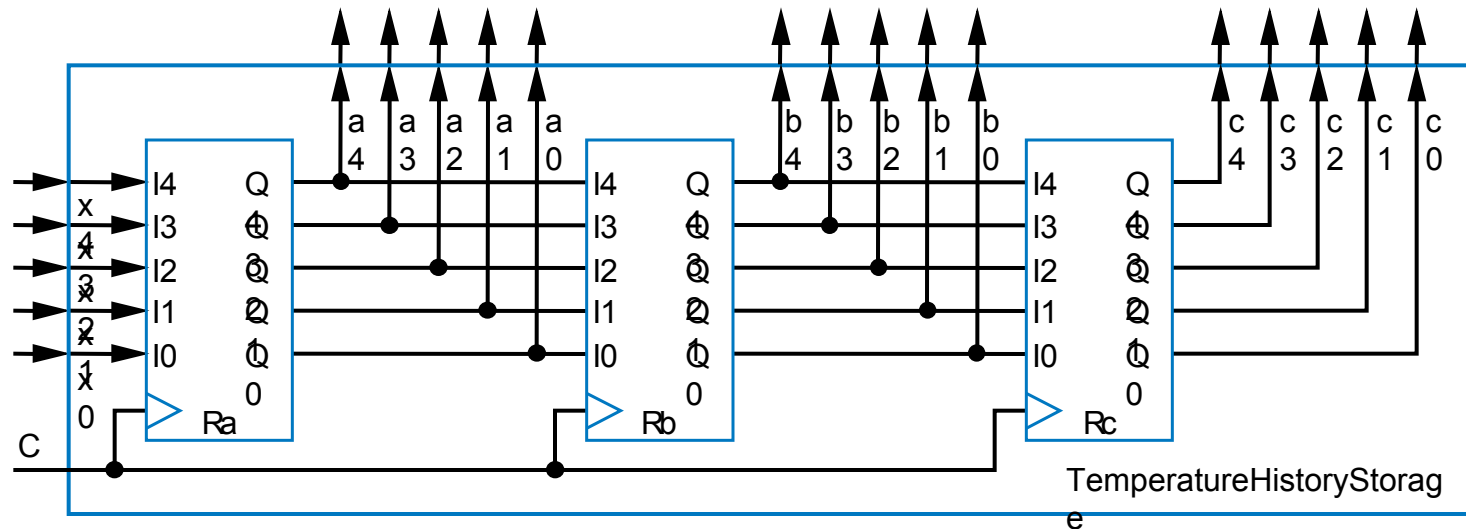

Register Example: Above-Mirror Display

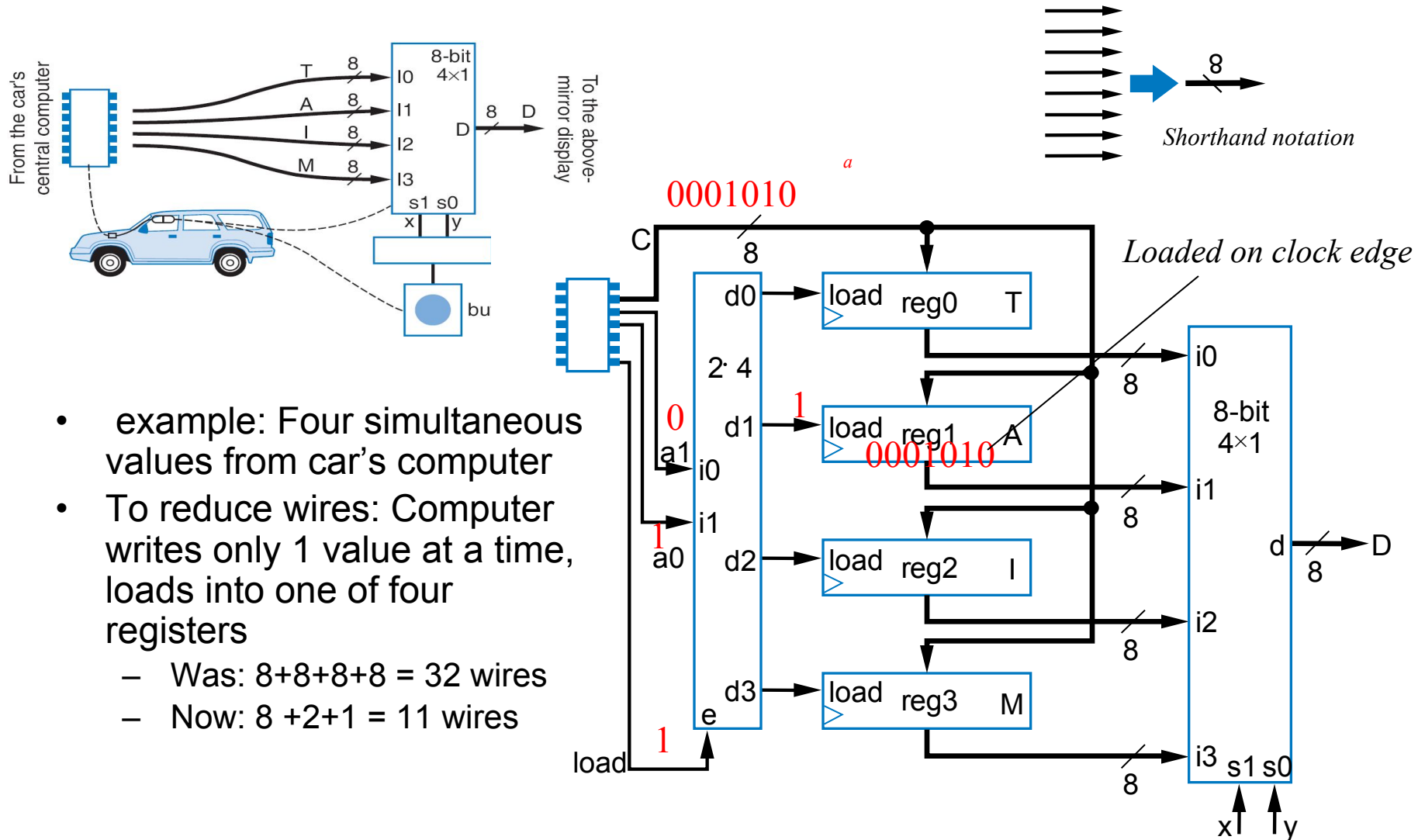


- example: Four simultaneous values from car's computer
- To reduce wires: Computer writes only 1 value at a time, loads into one of four registers
 - Was: $8+8+8+8 = 32$ wires
 - Now: $8 + 2 + 1 = 11$ wires


Shift Register Example: Above-Mirror Display

- Earlier example: 8 + 2 + 1 = 11 wires from car's computer to above-mirror display's four registers

 
- Better than 32 wires, but 11 still a lot -- want fewer for smaller wire bundles



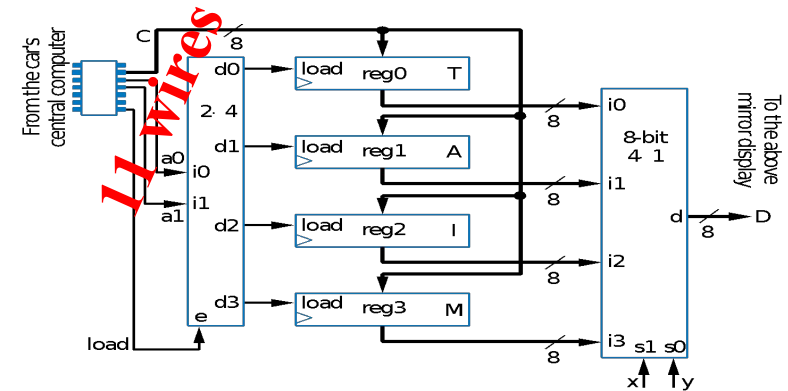- Use shift registers
 - Wires: 1 + 2 + 1 = 4
 - Computer sends one value at a time, one bit per clock cycle





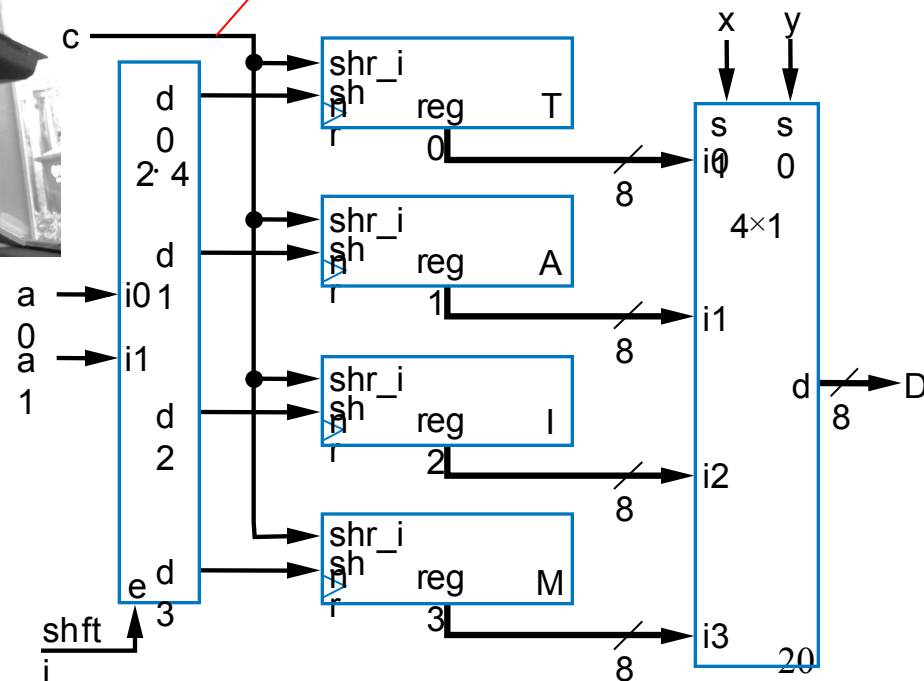Note: this line is 1 bit, rather than 8 bits like before



Rotate Register

  - Rotate right: Like shift right, but leftmost bit comes from rightmost bit





Multifunction Registers


- Many registers have multiple functions
 - Load, shift, clear (load all 0s)
 - And retain present value, of course
- Easily designed using muxes
 - Just connect each mux input to achieve desired function

Functions:


s1	s0	Operation
0	0	Maintain present value
0	1	Parallel load
1	0	Shift right
1	1	(unused - let's load 0s)

  

Universal Shift Registers

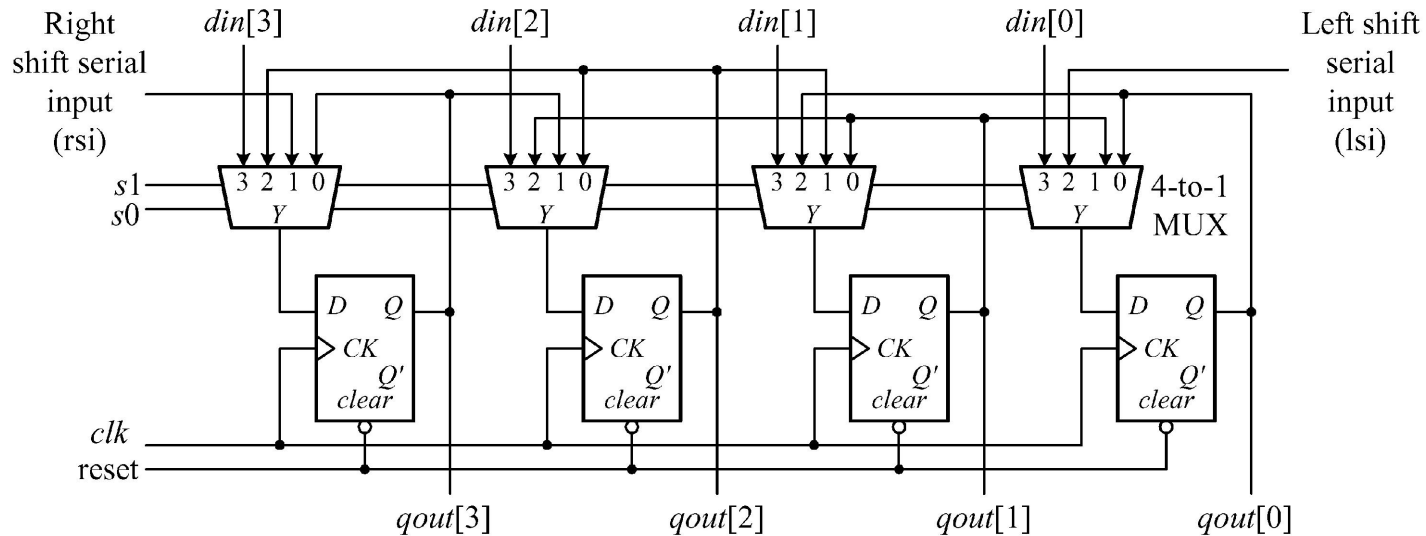

(a) Logic diagram

 




(b) Logic symbol

s1	s0	Function
0	0	No change
0	1	Right shift
1	0	Left shift
1	1	Load data

   
(c) Function table

Register File

- Instead, want component that has one data input and one data output, and allows us to specify which internal register to write and which to read



a

 

Register File Timing Diagram

- Can write one register and read one register each clock cycle
 - May be same register

