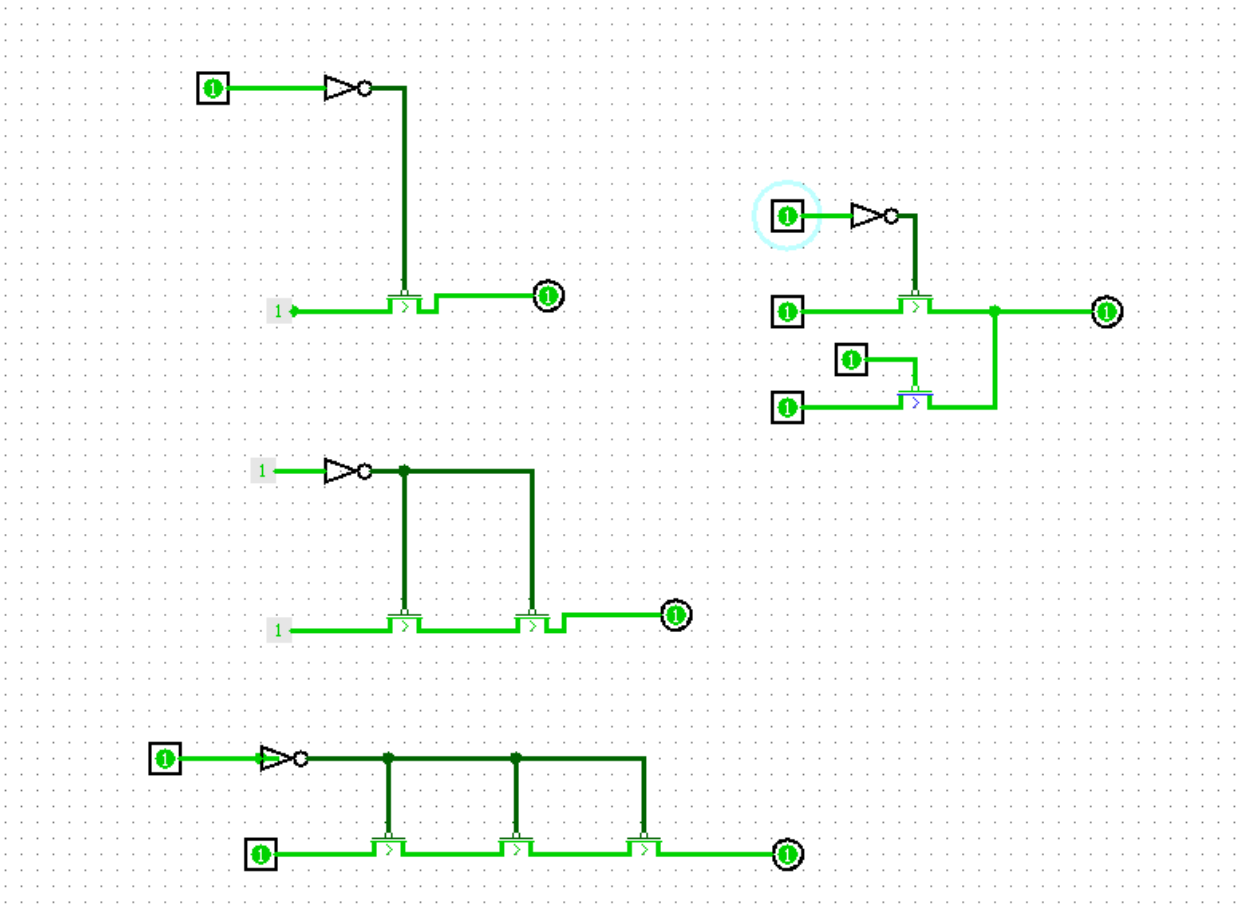


**Lab 2: Logic simulation Sub-blocks**


Exercise 1 (series parallel structures):

Simulate the following structures:

(Follow Lab1 steps to simulate)



Exercise 2 (NMOS gates):

 

### Assignment:

(Design and simulate)

1. Create series structure with 4 PMOS/NMOS transistors and verify the functionality (Assume A, B, C, and D are the inputs).  
(5 points)
2. Using NMOS logic, create 5 input NAND, NOR, AND and OR gates. (10 points)
3. Implement the following using CMOS Logic.  
$$Y = \overline{AB + CD + E}$$
(10 points)
4. Implement the following using CMOS Logic.  
$$Y = AB + CD + E$$
(5 points)
5. Create a library of gates (NAND, NOR, AND, OR, XOR) from the Lab 1 and implement the following using your library (See tutorial sub-circuits).  $Y = AB + C$  (15 points)
6. Implement and verify the functionality using existing library of Gates in logic-sim  
 $Y = A + BC + D$  (5 points)
7. Using CMOS logic, create 6 input NAND, NOR, and gates. (10 points)

### Submission:

.

Submit Report with hand drawn schematic is required for the problems (by end of the class). Show the simulations to TAs. Submit your .circ file containing your various transistor-level/logic level implementations

- The simulation files p1.circ, p2.circ, p3.circ, p4.circ, p5.circ and p6.circ
- Zip the above five files. Zip file name is your role number.

Course work submission through Email: [cs225.iitp@gmail.com](mailto:cs225.iitp@gmail.com)

(use email subject Lab2\_Logicsim\_your roll number).

This work is due on: 21<sup>st</sup> January