
 



# Memory

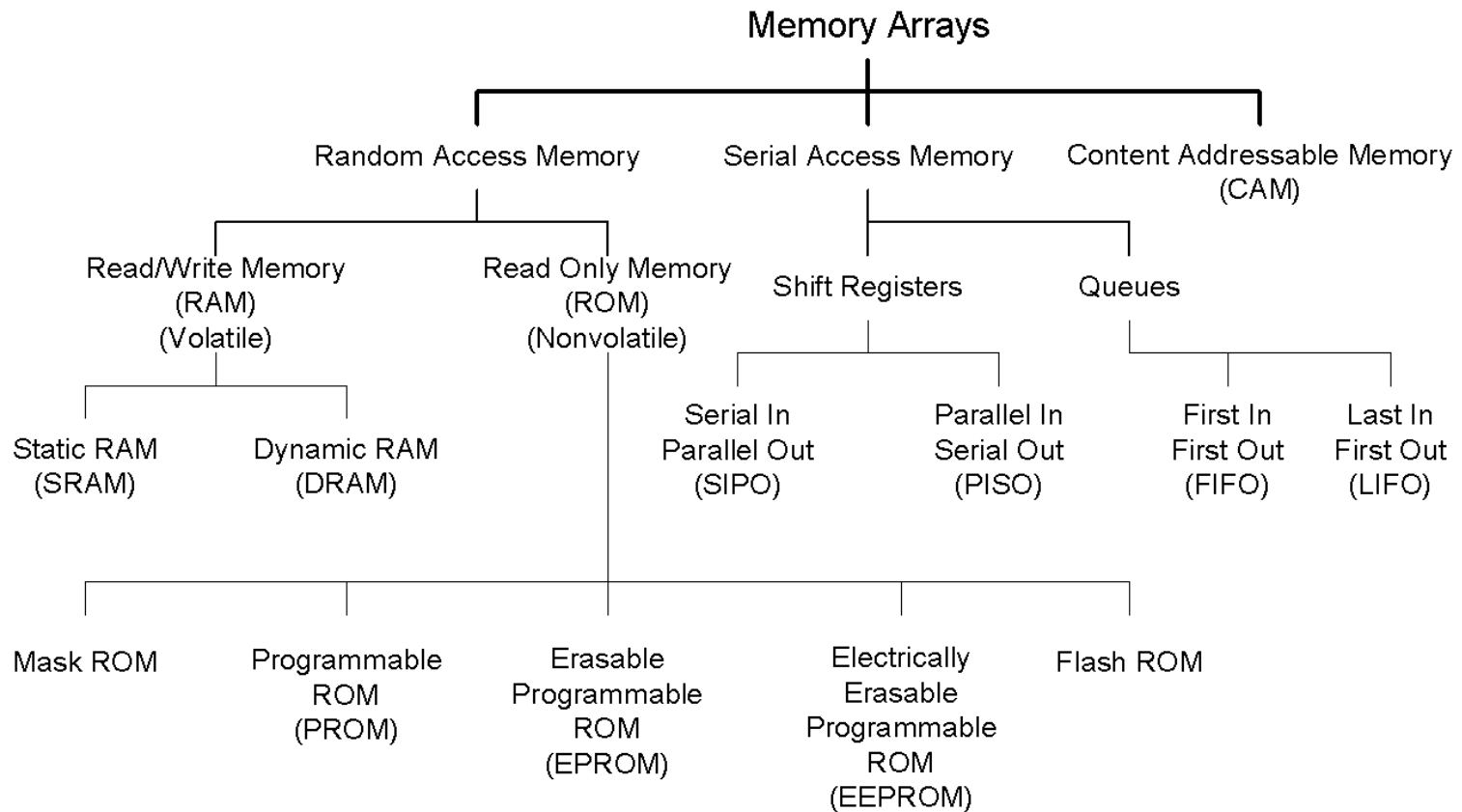

# Memory




# RAM

 

# Memory

64x8 RAM

Address	Data
000000	00111110
000001	01101011
000010	01011101
000011	01100011
000100	00111110
000101	00000000
000110	11111111
000111	01010101
001000	10101010
001001	00100001
001010	11011010

 

# 8x4 RAM

Address

Data

000

001

010

011

100

101

110

111


A2

A1

A0




# 8x4 RAM

 

 
# Static RAM Organization

Chip Select Line (active lo)  
Write Enable Line (active lo)  
10 Address Lines  
4 Bidirectional Data Lines



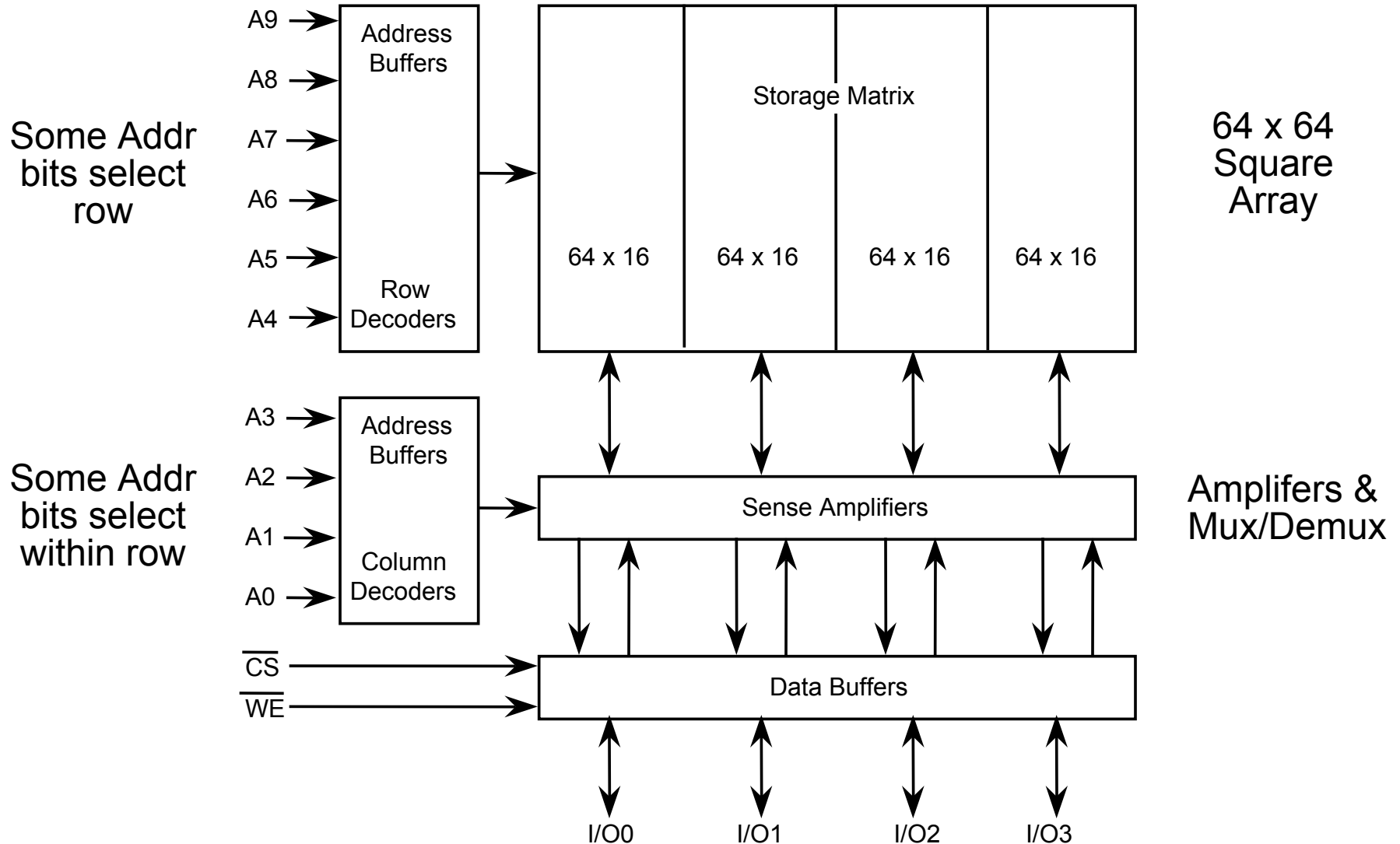
# RAM Organization

Long thin layouts are not the best organization for a RAM






# Processor Array

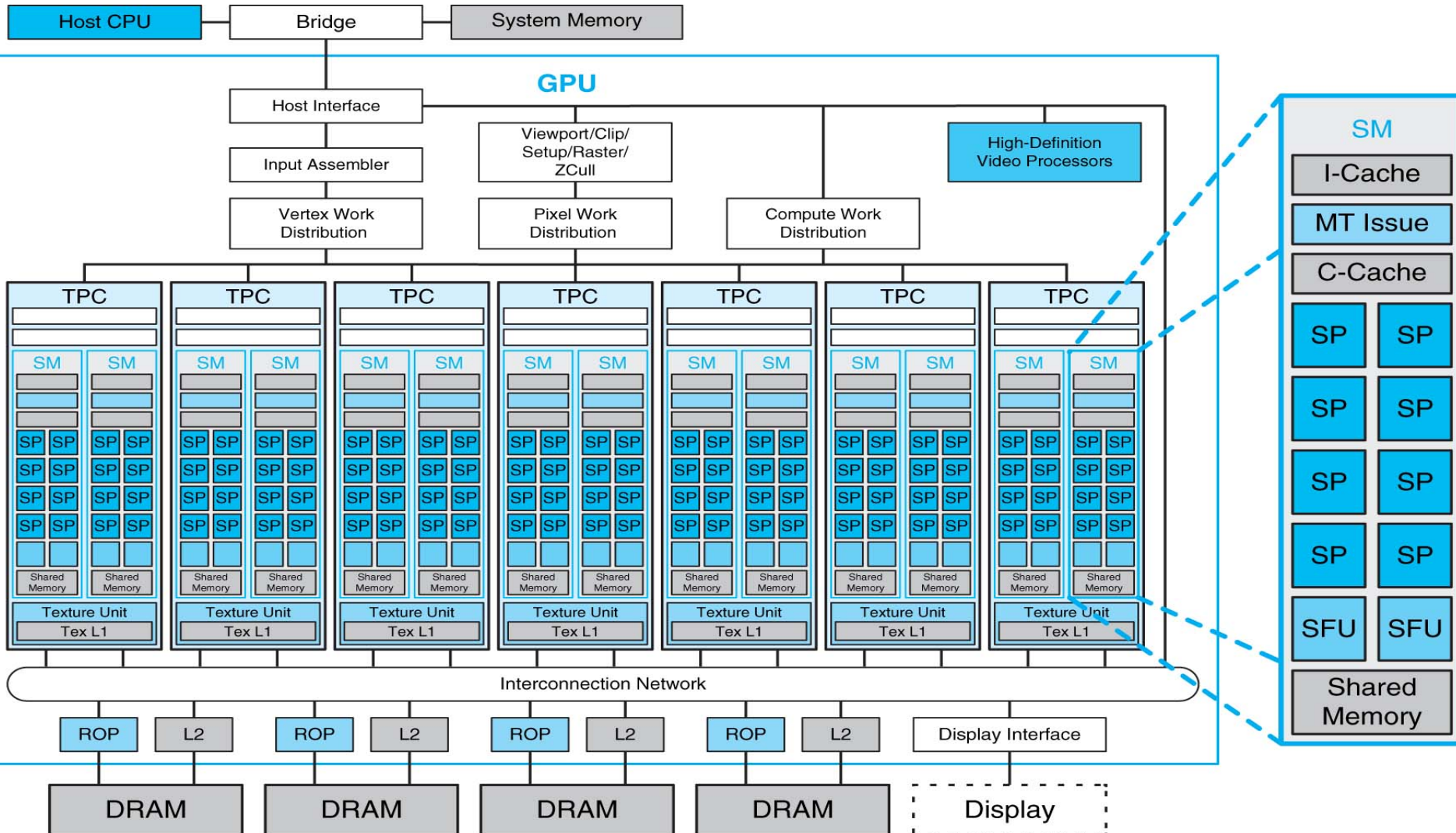


# 1Kx 1 bit RAM Organization

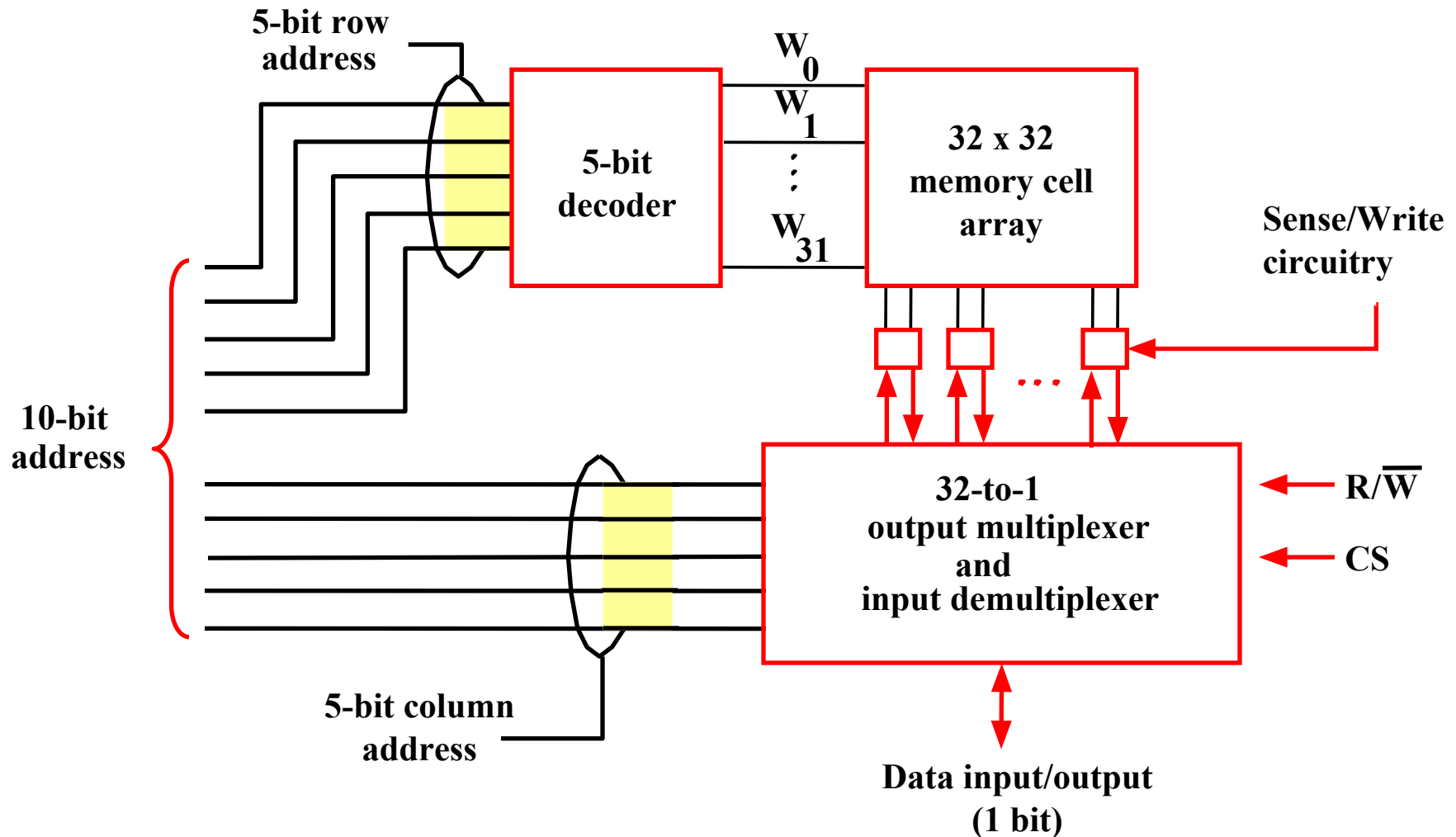

Organization of a  $1K \times 1$  memory chip.
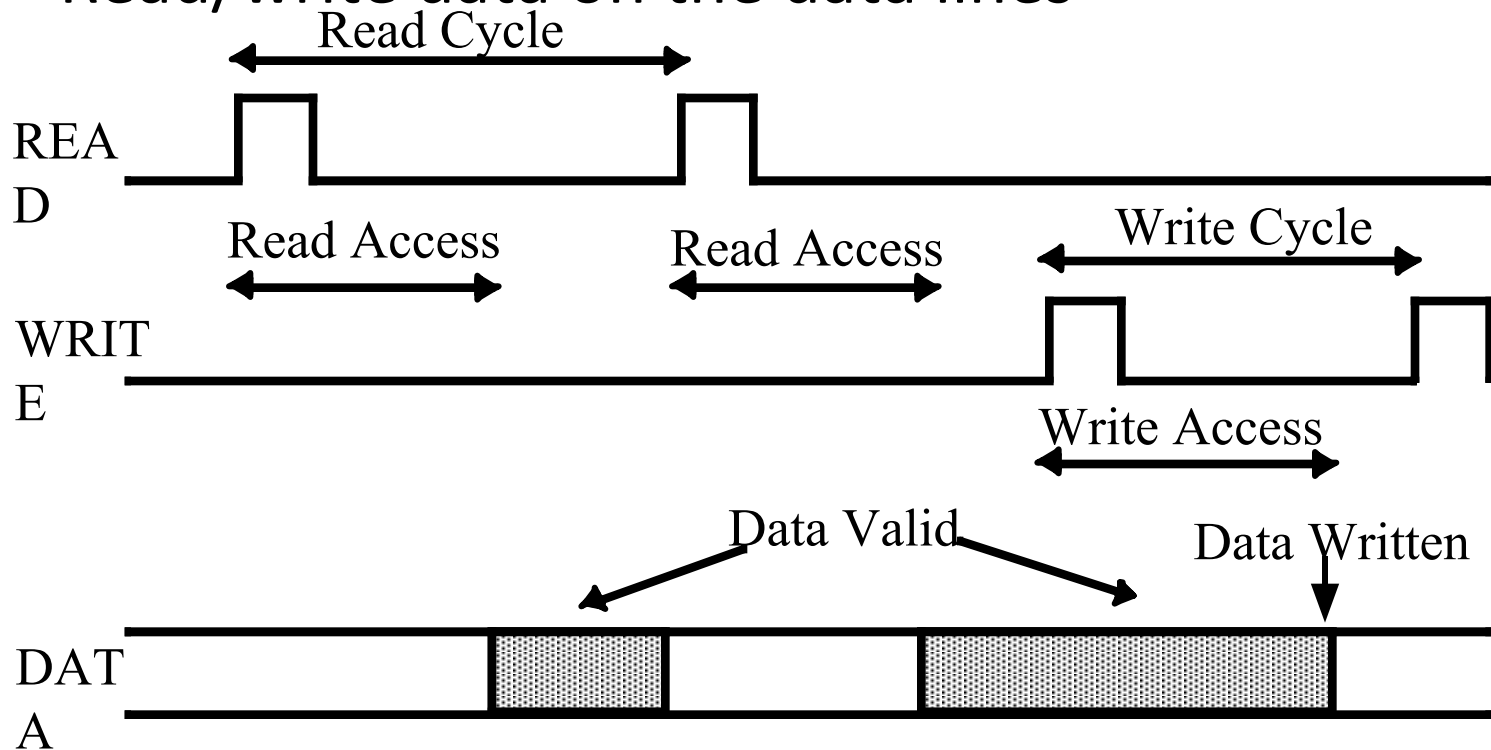
# Memory Access Timing: the Big Picture

- Timing:
  - Send address on the address lines, wait for the word line to become stable
  - Read/write data on the data lines



# Content of a memory

- Each **word in memory** is assigned an **identification number**, called an **address**, starting **from 0 up to  $2^k-1$** , where **k** is the **number of address lines**.
- The number of words in a memory with one of the letters  $K=2^{10}$ ,  $M=2^{20}$ , or  $G=2^{30}$ .

$$64K = 2^{16} \quad 2M = 2^{21}$$


$$4G = 2^{32}$$

Memory address		Memory content
Binary	decimal	
0000000000	0	1011010101011101
0000000001	1	1010101110001001
0000000010	2	0000110101000110
	⋮	⋮
1111111101	1021	1001110100010100
1111111110	1022	0000110100011110
1111111111	1023	1101111000100101

1024x16 Memory Module

 
# Memory Cell Array Access Example

- word=16-bit wide(N), row=8 words(L), address=10 bits (k)
- Accessing word 9=  $0000001001_2$



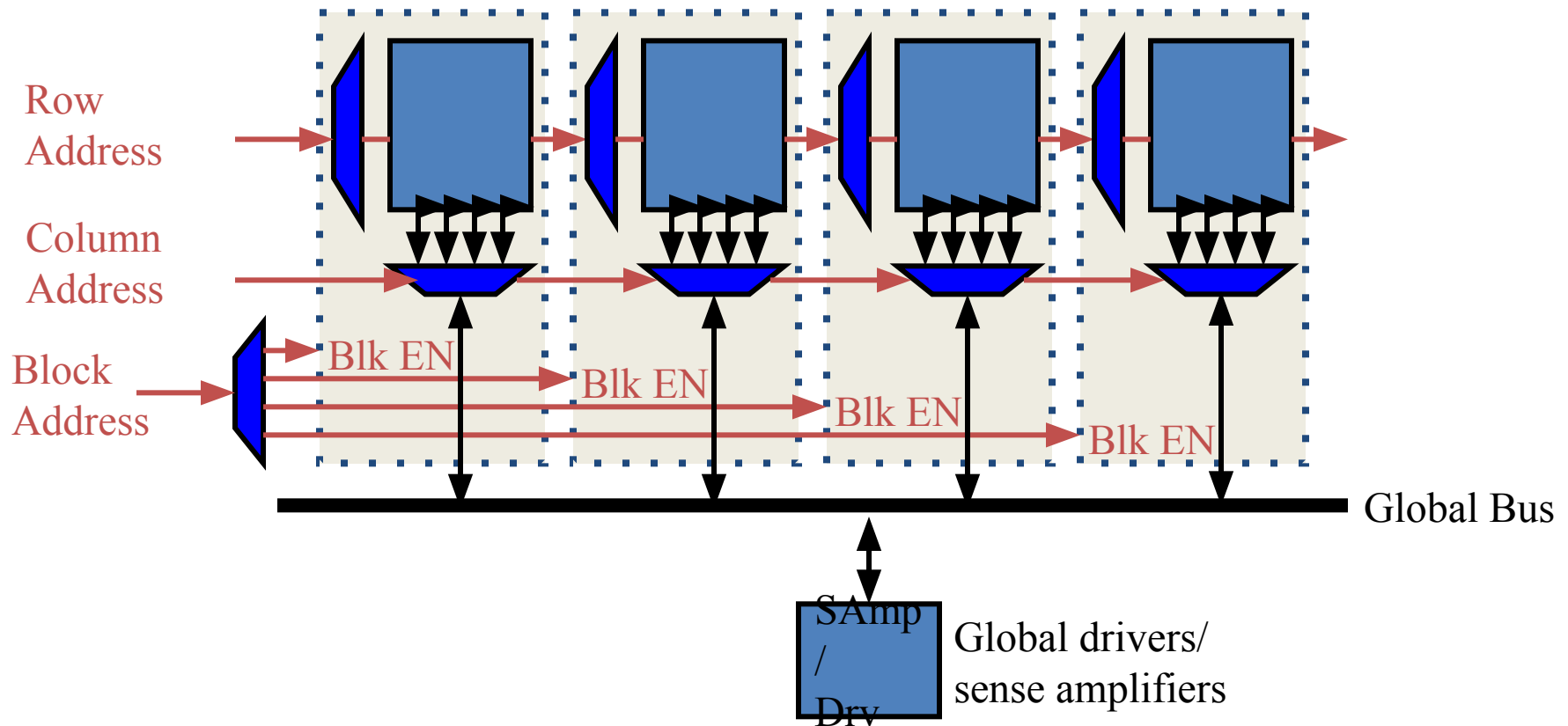
# Memory Structures


- Taking the idea one step further
  - Shorter wires within each block
  - Enable only one block addr decoder power savings



# Larger Memories Using Multiple Chips

 


Question ? Design a 2Mx32 given: 512Kx8

 


Organization of a  $2M \times 32$  memory module using  $512K \times 8$  static memory chips (16 chips).



## 19-bit internal chip address

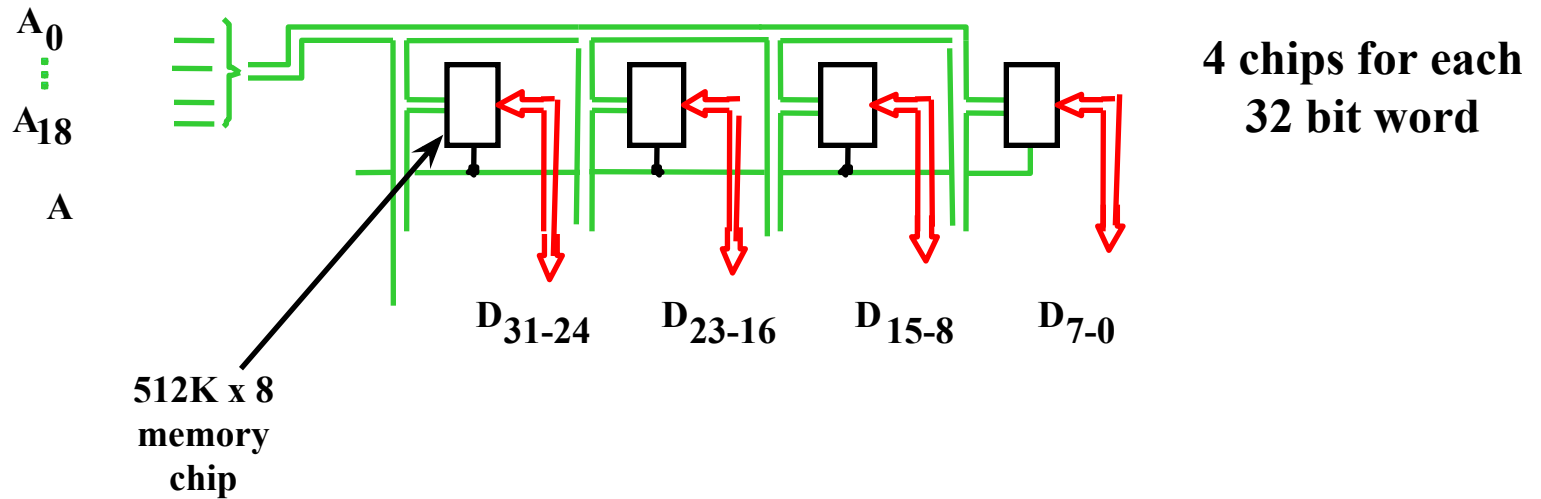


 
Organization of a  $2M \times 32$  memory module using  $512K \times 8$  static memory chips (16 chips).



Organization of a  $2M \times 32$  memory module using  $512K \times 8$  static memory chips (16 chips).
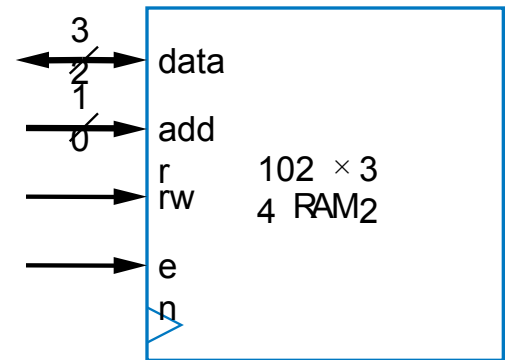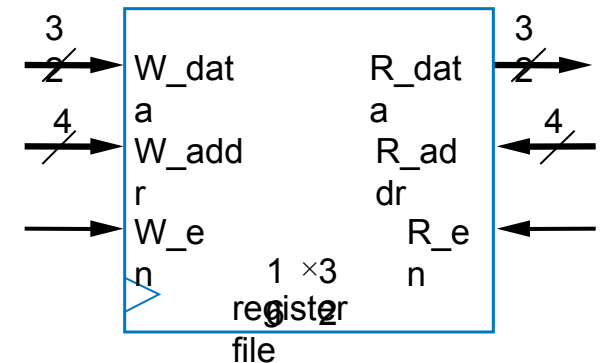
# Random Access Memory (RAM)


- RAM – Readable and writable memory
  - “Random access memory”
    - Strange name—Created several decades ago to contrast with sequentially-accessed storage like tape drives
  - Logically same as register file—Memory with address inputs, data inputs/outputs, and control
    - RAM usually one port; RF usually two or more
  - RAM vs. RF
    - RAM typically larger than *about* 512 or 1024 words
    - RAM typically stores bits using a bit storage approach that is more efficient than a flip-flop
    - RAM typically implemented on a chip in a square rather than rectangular shape—keeps longest wires (hence delay) short




RAM block symbol
 
# Simplest circuits with feedback

- Two inverters form a static memory cell
  - will hold value as long as it has power applied




 - How to get a new value into the memory cell?
  - selectively break feedback path
  - load new value into cell



 
# Implementing Registers in CMOS

- Uses transmission gate
  - When “WR” asserted, “write” operation will take place
  - Stack D latch structures to get n-bit register




# RAM Internal Structure

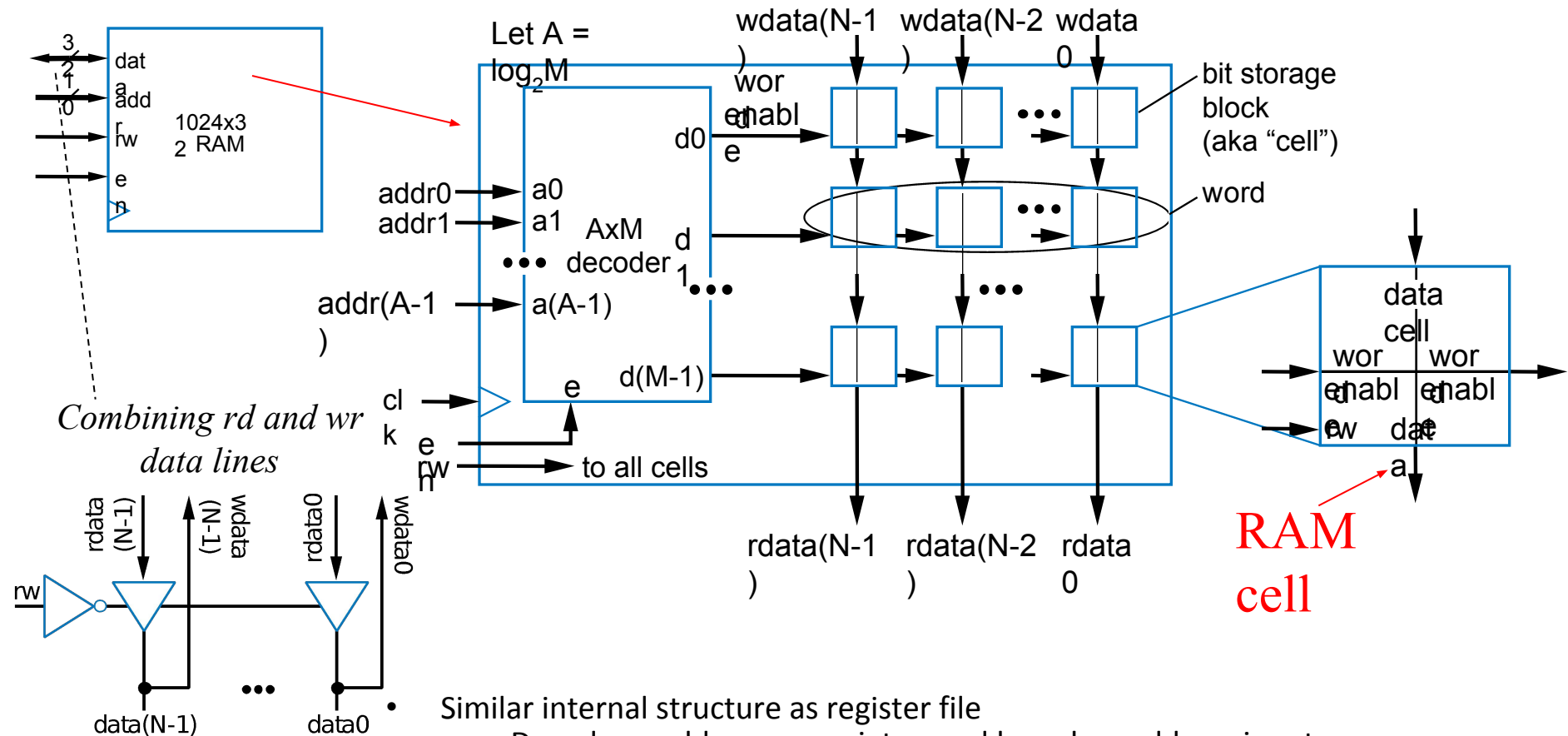


- Decoder enables appropriate word based on address inputs
- rw controls whether cell is written or read
- rd and wr data lines typically combined
- Let's see what's inside each RAM cell

# Static RAM (SRAM)


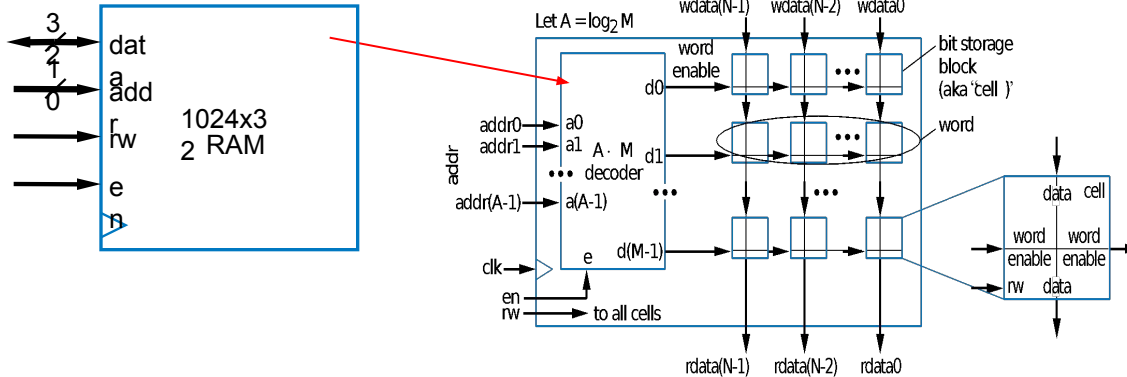


- “Static” RAM cell
  - 6 transistors (recall inverter is 2 transistors)
  - Writing this cell
    - *word enable* input comes from decoder
    - When 0, value *d* loops around inverters
      - That loop is where a bit stays stored
    - When 1, the *data* bit value enters the loop
      - *data* is the bit to be stored in this cell
      - *data'* enters on other side
      - Example shows a “1” being written into cell


SRAM cell

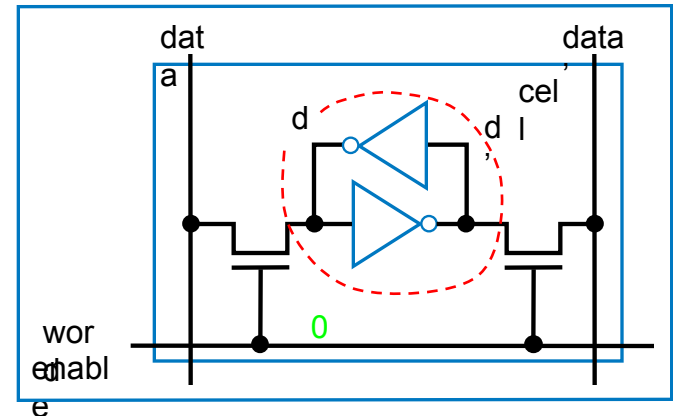

SRAM cell

  


# Static RAM (SRAM)

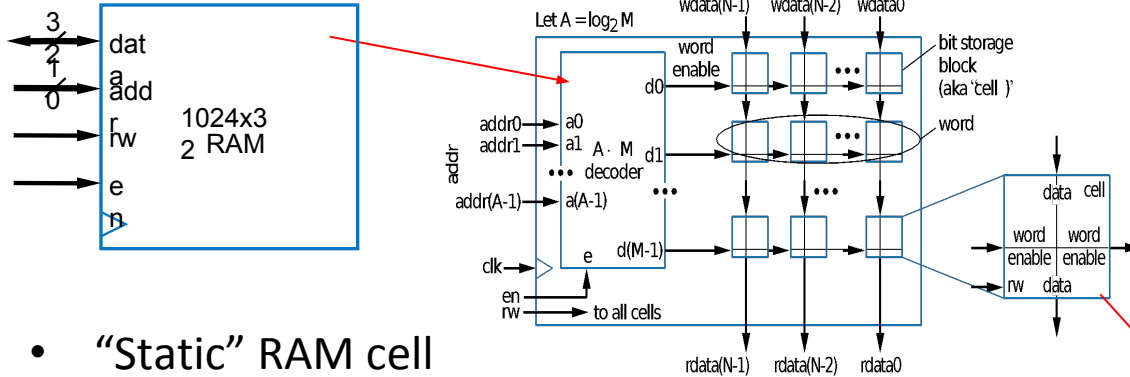

- “Static” RAM cell
  - Reading this cell
    - Somewhat trickier
    - When rw set to read, the RAM logic sets both *data* and *data'* to 1
    - The stored bit *d* will pull either the left line or the right bit down slightly below 1
    - “Sense amplifiers” detect which side is slightly pulled down
  - The electrical description of SRAM is really beyond our scope – just general idea here, mainly to contrast with *DRAM*...



## SRAM cell

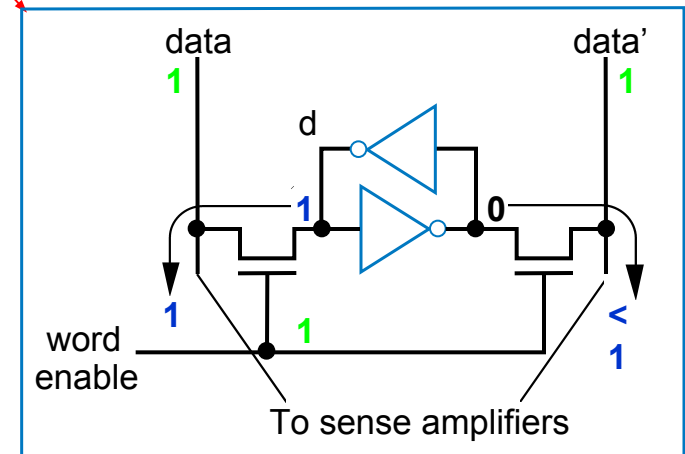




# SRAM Column Example


Read

  

Write

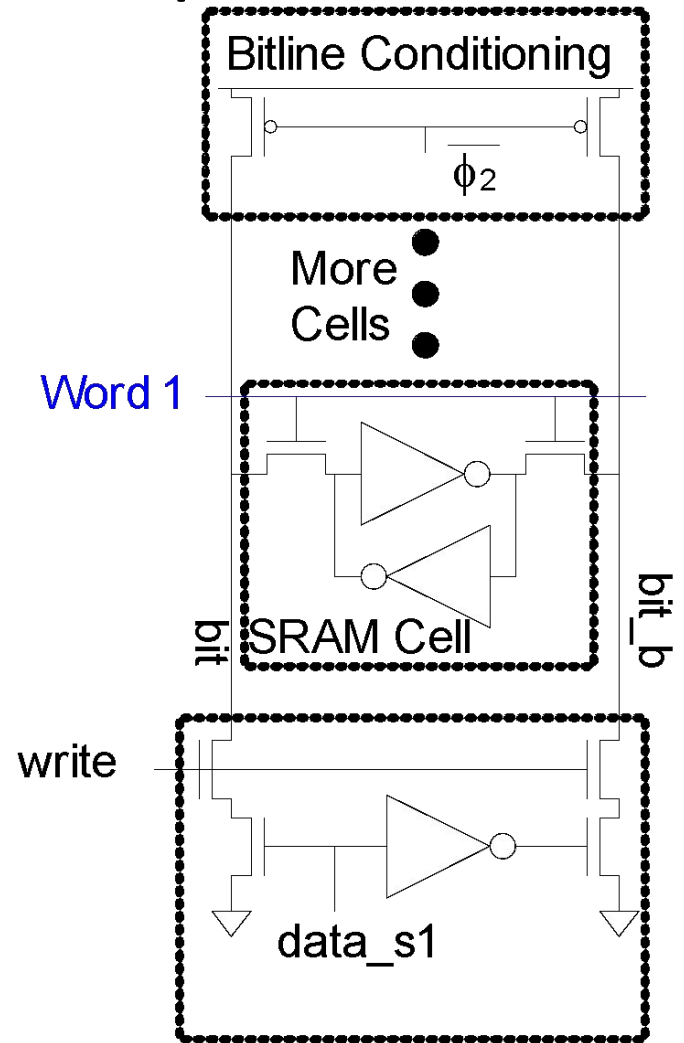

# Dynamic RAM (DRAM)

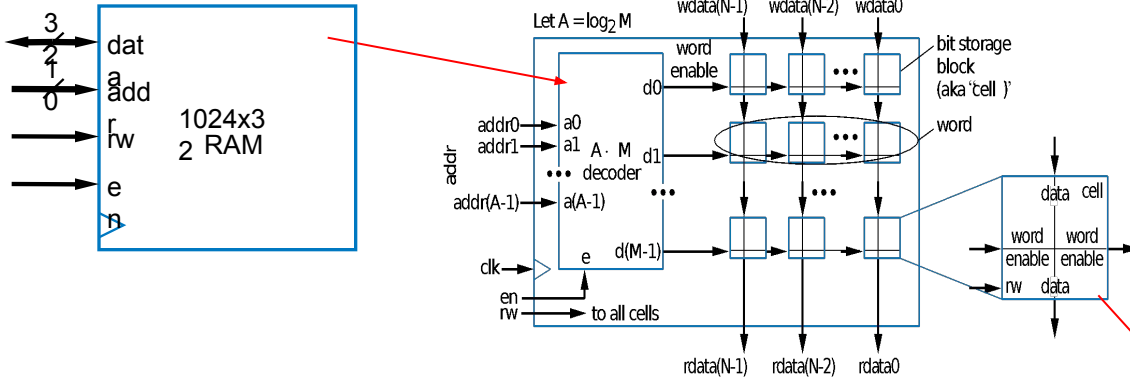


- “Dynamic” RAM cell

- 1 transistor (rather than 6)
- Relies on *large* capacitor to store bit

- Write: Transistor conducts, data voltage level gets stored on top plate of capacitor
- Read: Just look at value of  $d$
- Problem: Capacitor discharges over time
  - Must “refresh” regularly, by reading  $d$  and then writing it right back



# DRAM cell

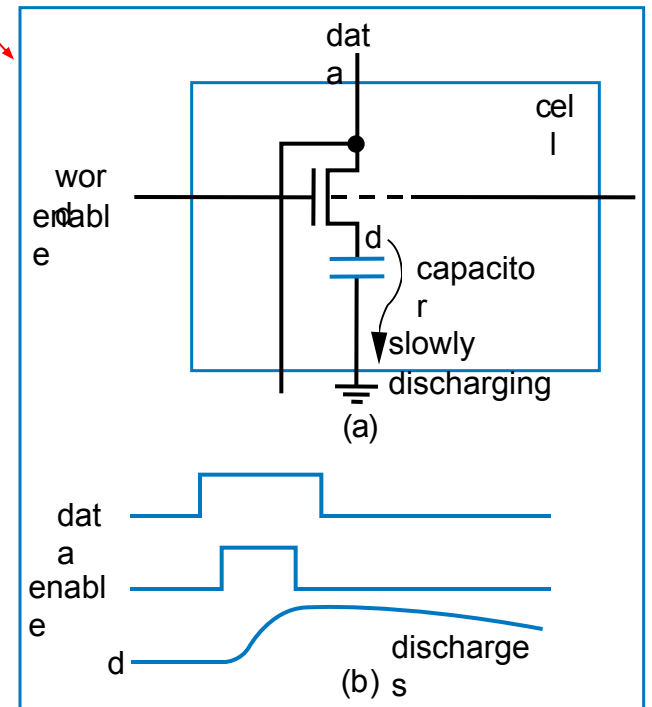

# Dynamic RAM (DRAM)


- “Dynamic” RAM cell
  - 1 transistor (rather than 6)
  - Relies on capacitor to store bit

DRAM cell

 
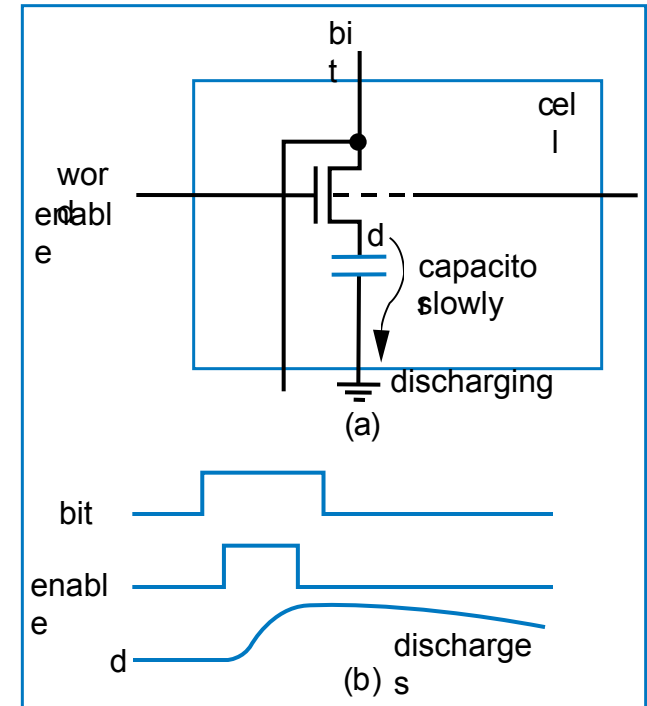


2014

# Dynamic RAM 1-Transistor Cell: Layout

 


Trench Cell

  


Stacked-capacitor Cell
 
# Comparing Memory


- Register file
  - Fastest
  - But biggest size
- SRAM
  - Fast
  - More compact than register file
- DRAM
  - Slowest (capacitor)
    - And refreshing takes time
  - But very compact (lower cost)
- Use register file for small items, SRAM for large items, and DRAM for huge items
  - Note: DRAM's big capacitor requires a special chip design process, so DRAM is often a separate chip



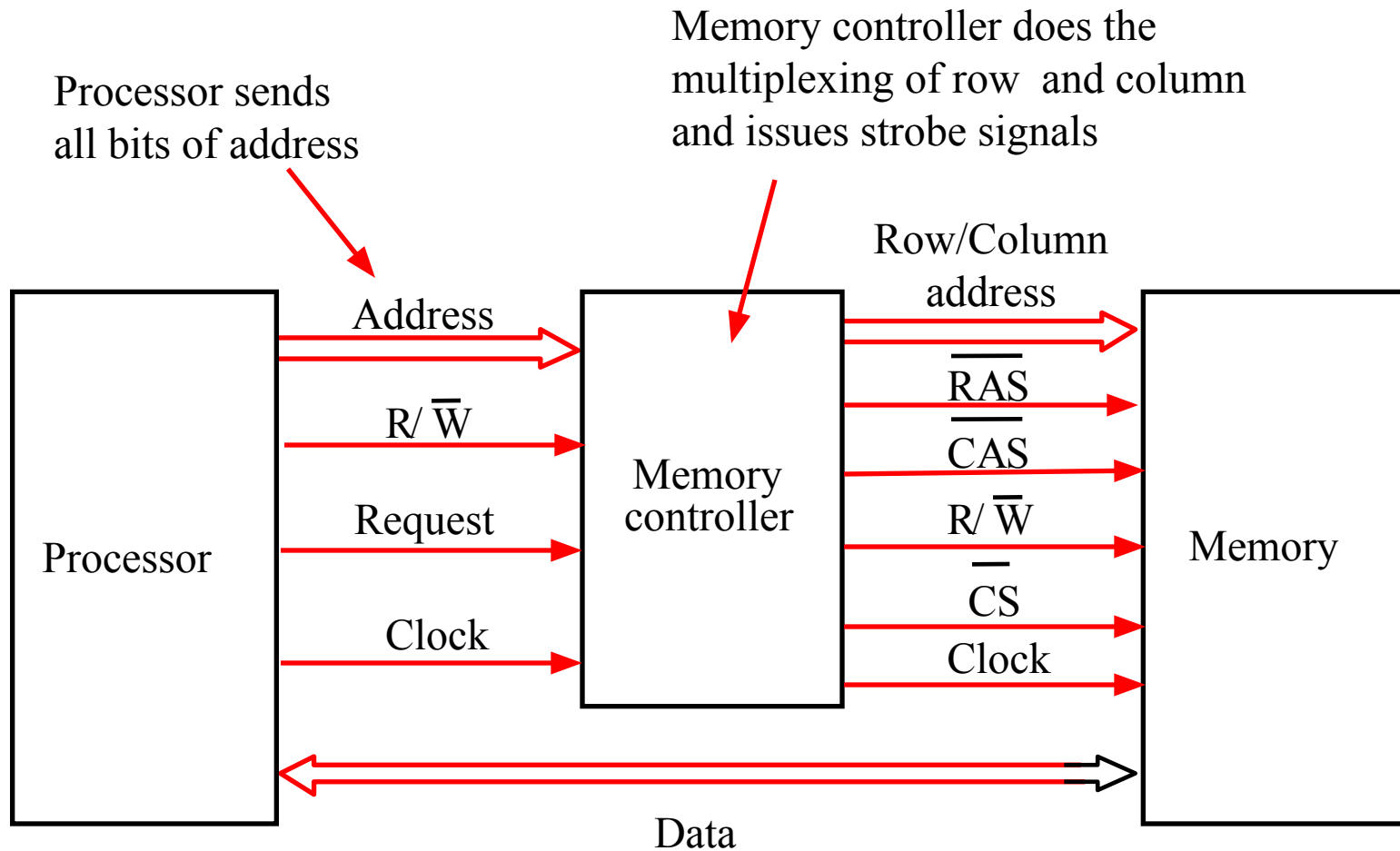Size comparison for same number of bits (not to scale)



Use of a memory controller.

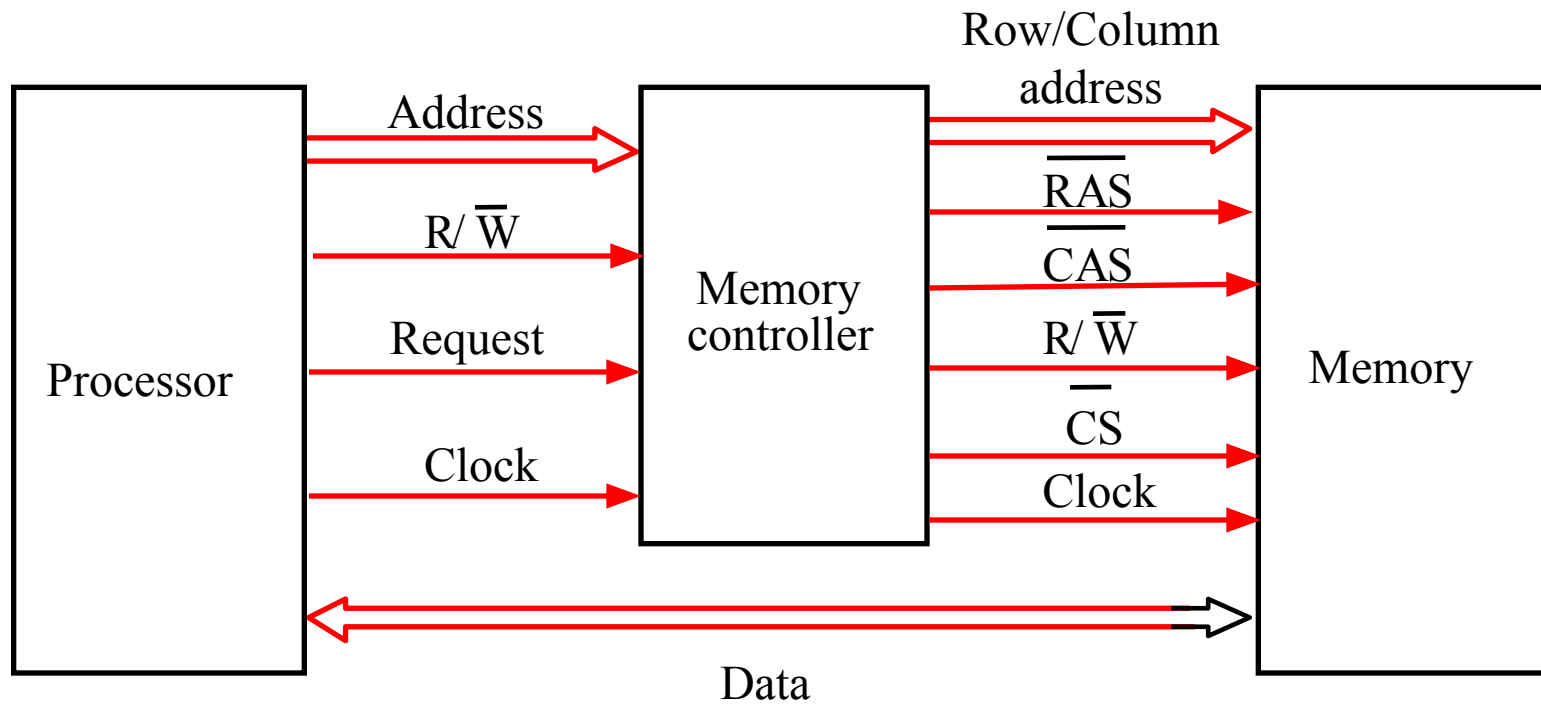

Memory controller provides the refresh control if not done on the chip

Refreshing typically once every 64 ms. At a cost of .2ms

Less than .4% overhead

Use of a memory controller.

# CAM

- CAM vs. RAM

