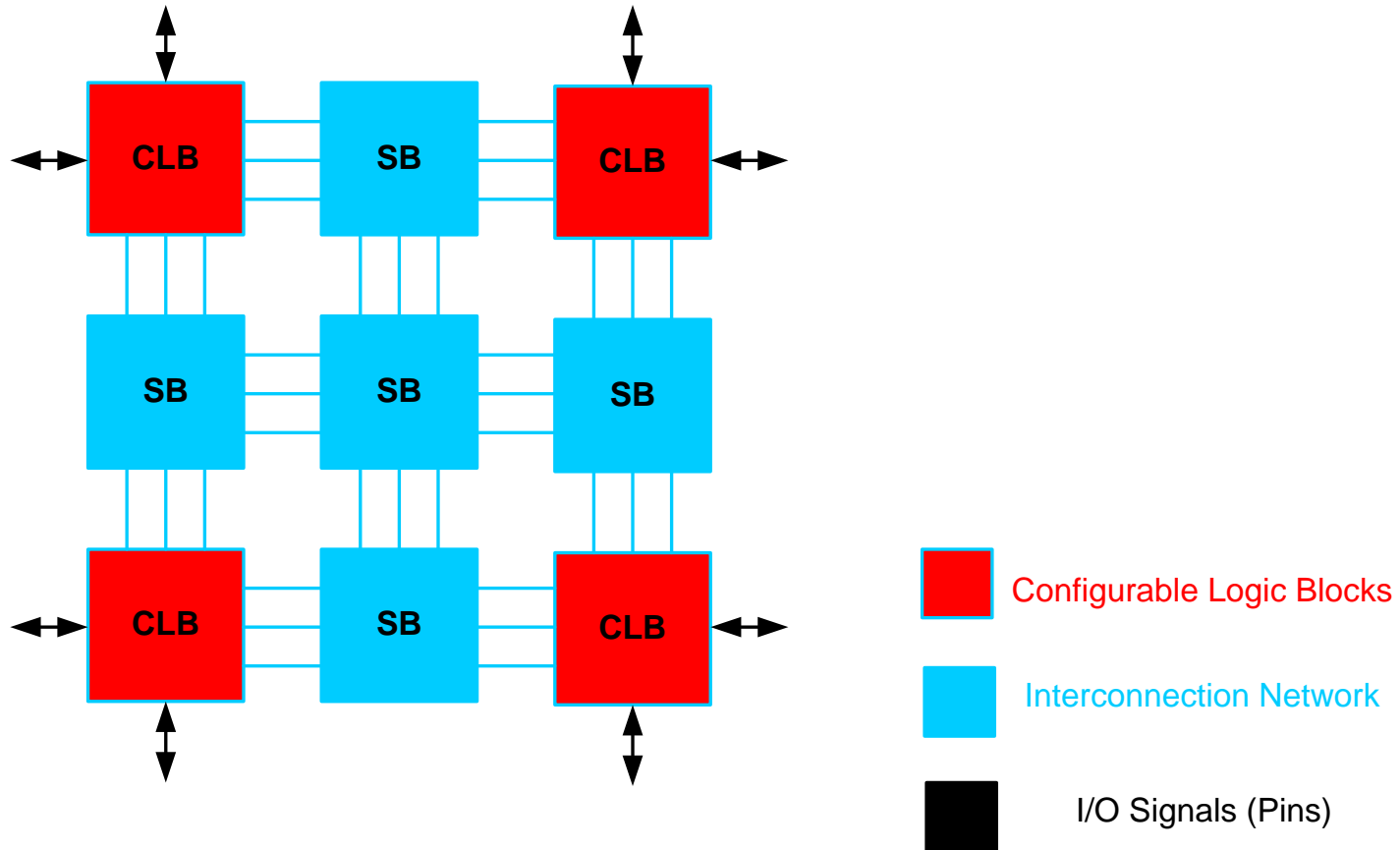


# Manufacturers


- Xilinx
- Altera
- Lattice
- Actel




# FPGA structure




# Simplified CLB Structure

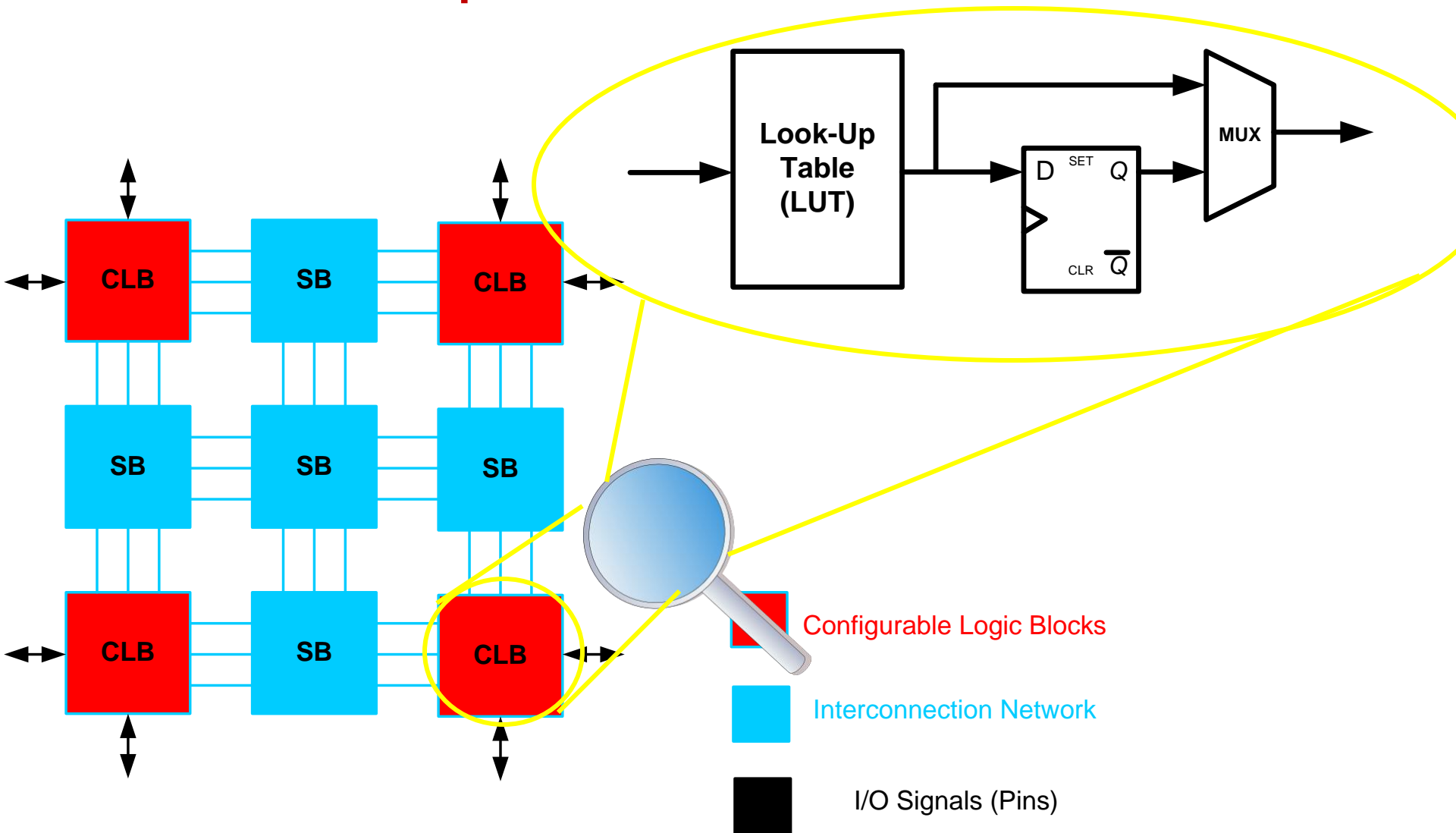


# Example: 4-input AND gate

 


A	B	C	D	O
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

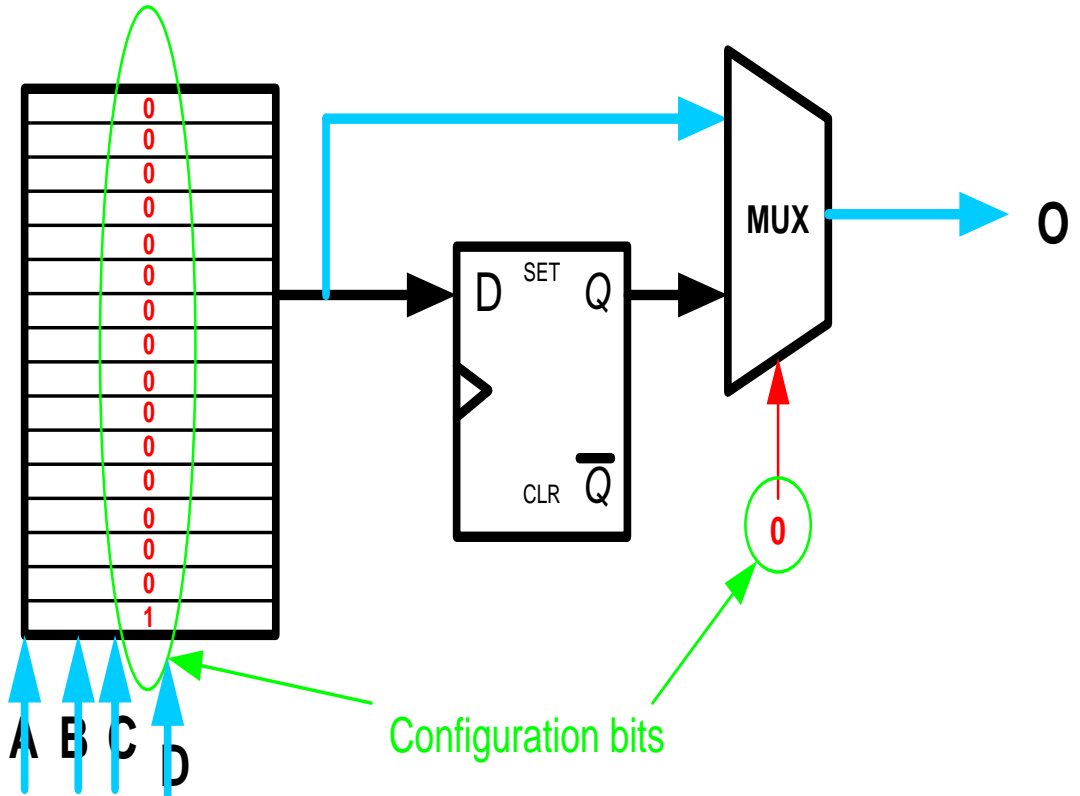

 
# Example 2: Find the configuration bits for the following circuit



A0	A1	S	
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

 


# Interconnection Network


 

 
# Example 3

- Determine the configuration bits for the following circuit implementation in a 2x2 FPGA, with I/O constraints as shown in the following figure. Assume 2-input LUTs in each CLB.




# CLBs required


 
 




# Placement: Select CLBs

 



# Routing: Select path

   

 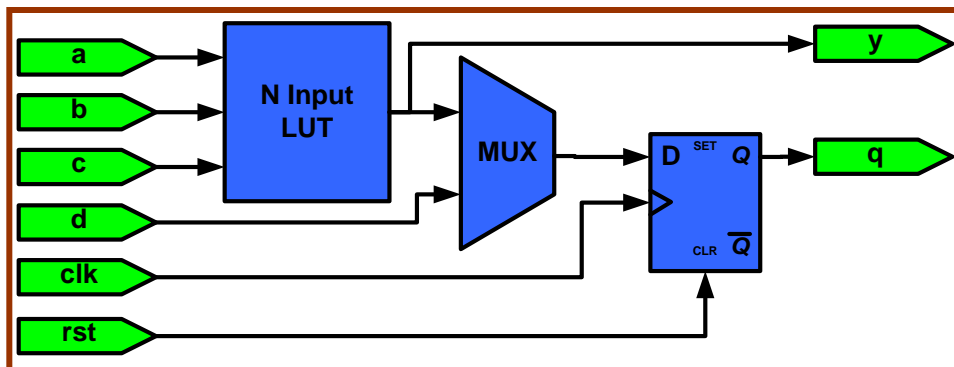
# Configuration Bitstream

- The configuration bitstream must include ALL CLBs and SBs, even unused ones
- CLB0: 00011
- CLB1: 01100
- CLB2: XXXXX
- CLB3: XXXXX
- SB0: 000000
- SB1: 000010
- SB2: 000000
- SB3: 000000
- SB4: 000001


- Programmable logic blocks (Logic Element “LE”)  
Implement combinatorial and sequential logic. Based on LUT and DFF.
- Programmable I/O blocks  
Configurable I/Os for external connections supports various voltages and tri-states.
- Programmable interconnect  
Wires to connect inputs , outputs and logic blocks.
  - clocks
  - short distance local connections
  - long distance connections across chip



# Realistic FPGA CLB: Xilinx

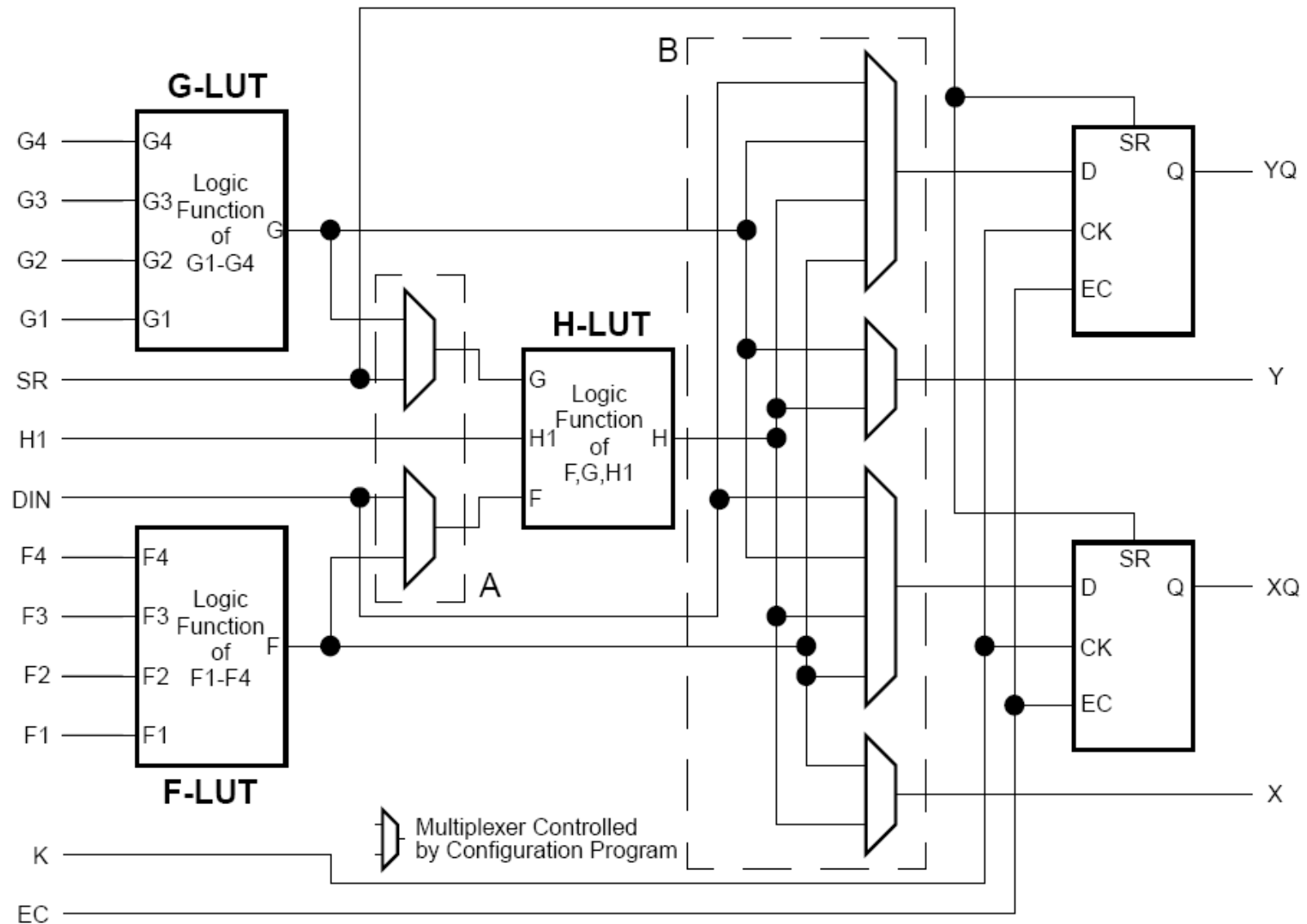

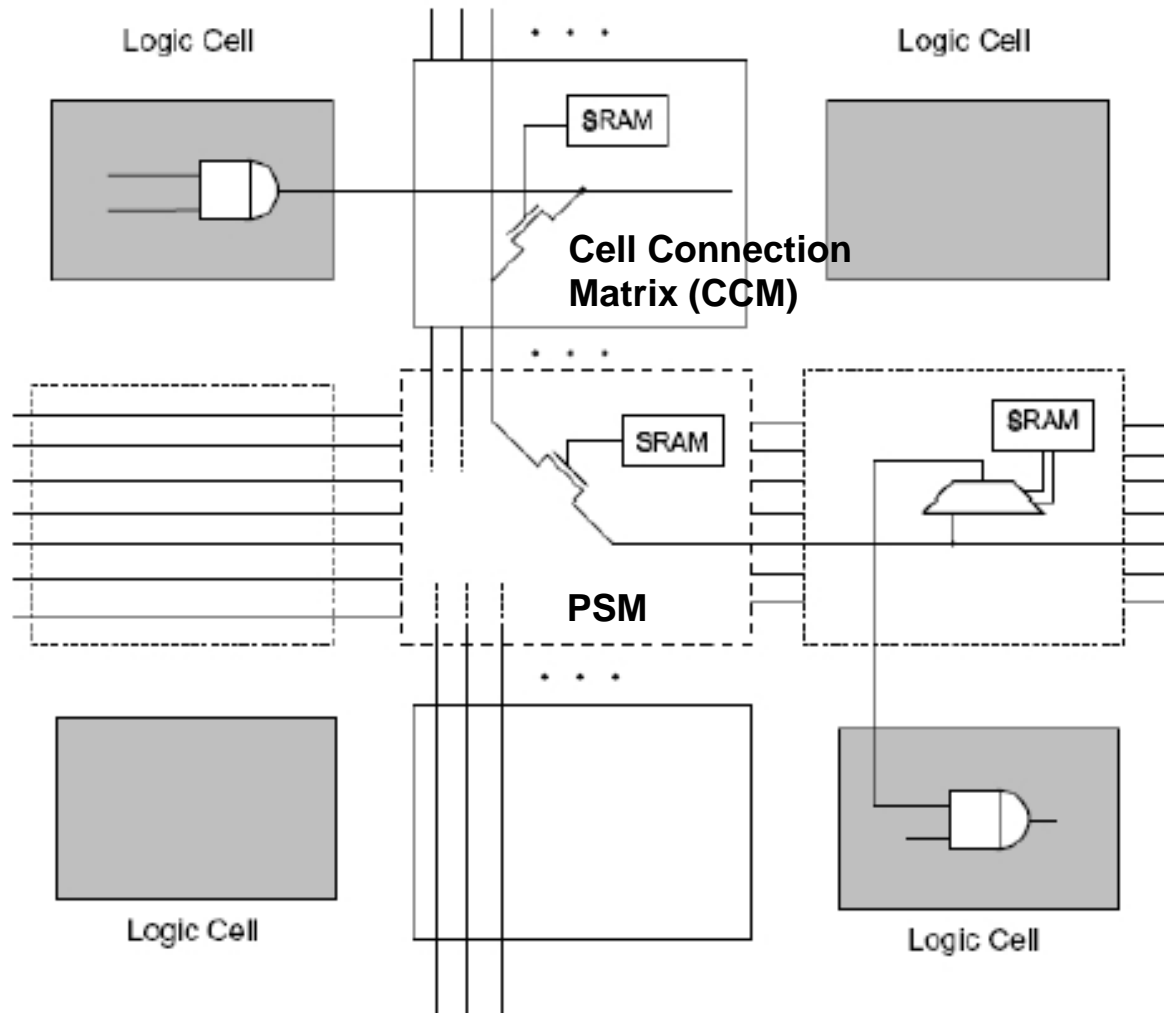
# SRAM-type FPGA Interconnect Architecture (contd)



# Configuration Logic Block (CLB)

## XC4000E CLB

- ✉ 2 Four-input function generators (Look Up Tables)
- ✉ 1 Three-input function
- ✉ 2 Registers:
  - Pos. or Neg. edge-trig. Synchronous and asynchr. Set/Reset
- ✉ Possible functions:
  - any fct of 5 var.
  - two fcts of 4 var. + one fct of 3 var.
  - some fct of 9 var.

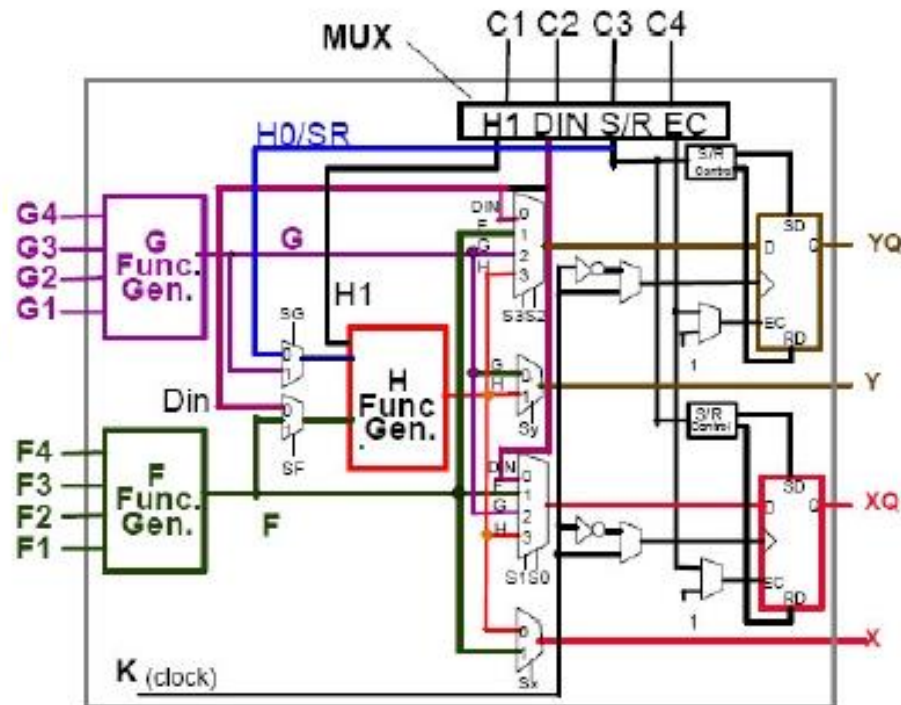

EE200

Figure courtesy of Xilinx, Inc. © Xilinx, Inc. 1996. All rights reserved

- 5-i/p function implemented using G, F and H LUTs (Look Up Tables) using *Shannon's Expansion*:  $p(a,b,c,d,e) = a p(1, b, c, d, e) + a' p(0, b, c, d, e) = a q(b,c,d,e) + a' r(b,c,d,e)$ .  
 $q()$  impl. using LUT G,  $r$  impl. using LUT F and  $p = ag + a'h$  impl. using LUT H
- The LUT o/p's can go through a FF (for seq. ckt design) or bypass it for a combinational o/p
- This is called *technology mapping*: mapping the logic to CLB logic components

# Mapping

## Example



- Implement the following functions on a single CLB of the XC4000 FPGA:

$$X = A'B'(C + D)$$

$$Y = AK + BK + C'D'K + AEJL$$


- Use look up table F to implement X
- Use look up table G for AEJL
- Use F, G and H for Y:

$$\begin{aligned} Y &= K(A+B + C'D') + AEJL \\ &= KX' + AEJL = KF' + G \end{aligned}$$




# Programming a CLB (contd)

## Example

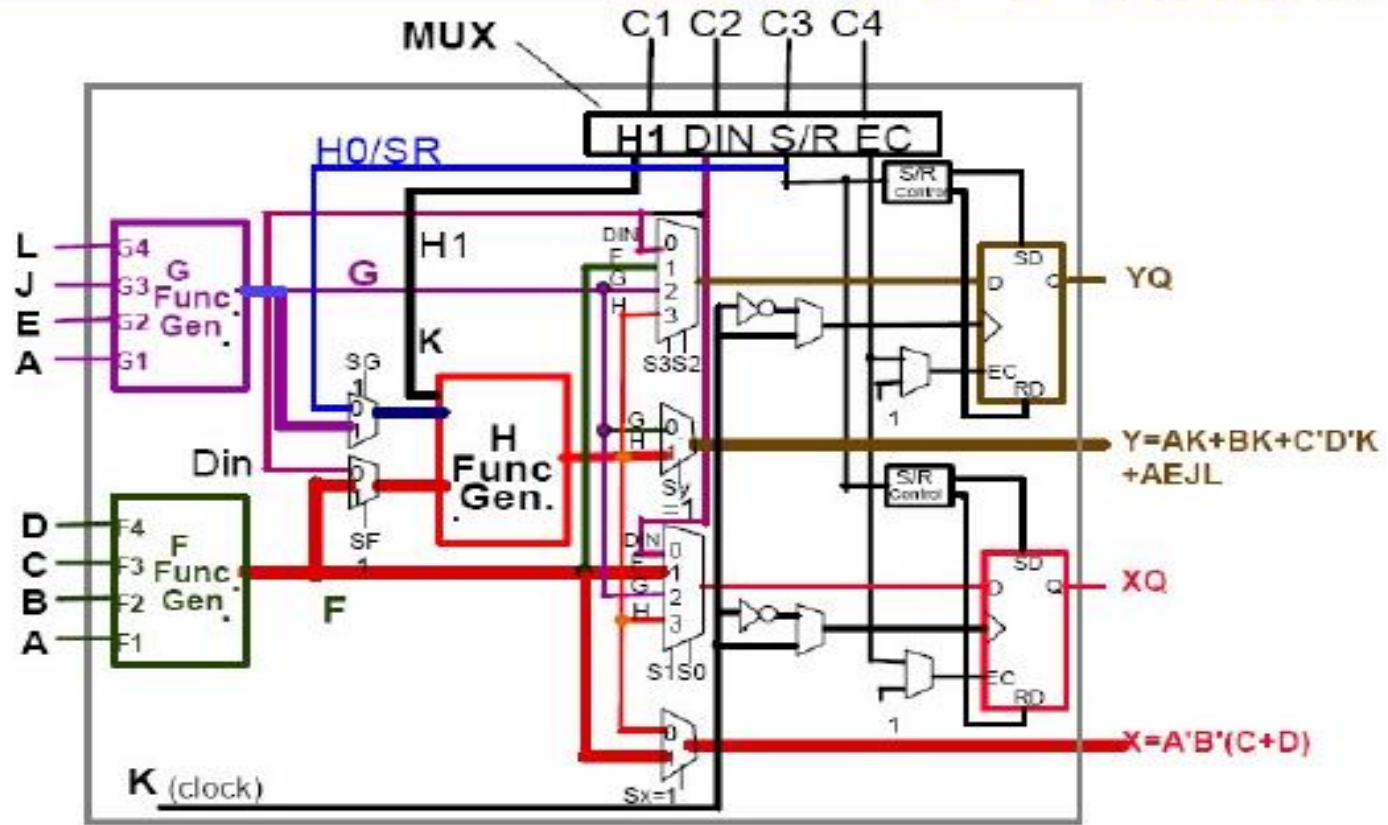

# Components of Modern FPGAs

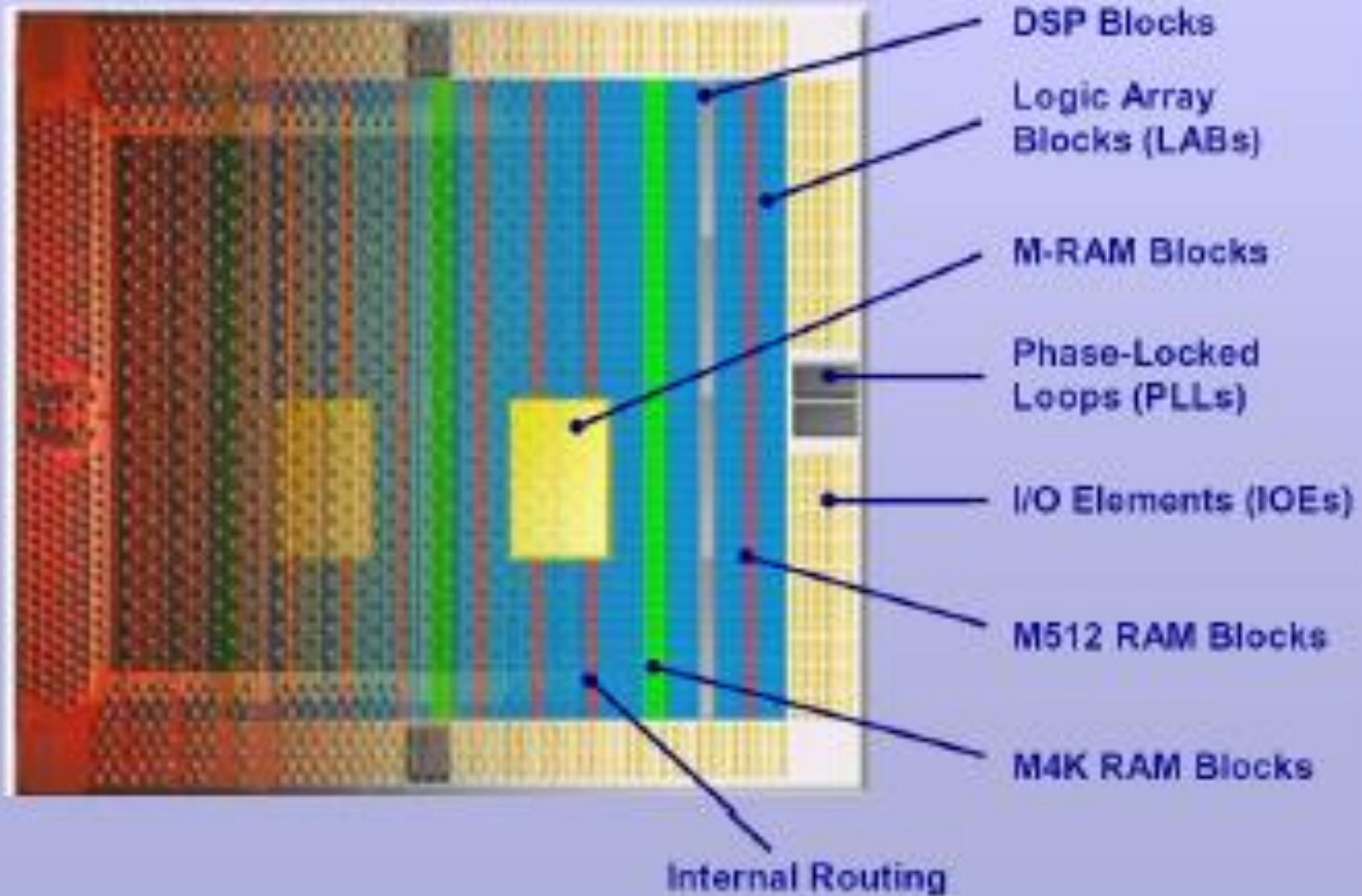


# FPGA EDA Tools

- Must provide a design environment based on digital design concepts and components (gates, flip-flops, MUXs, etc.)
- Must hide the complexities of placement, routing and bitstream generation from the user. Manual placement, routing and bitstream generation is infeasible for practical FPGA array sizes and circuit complexities.

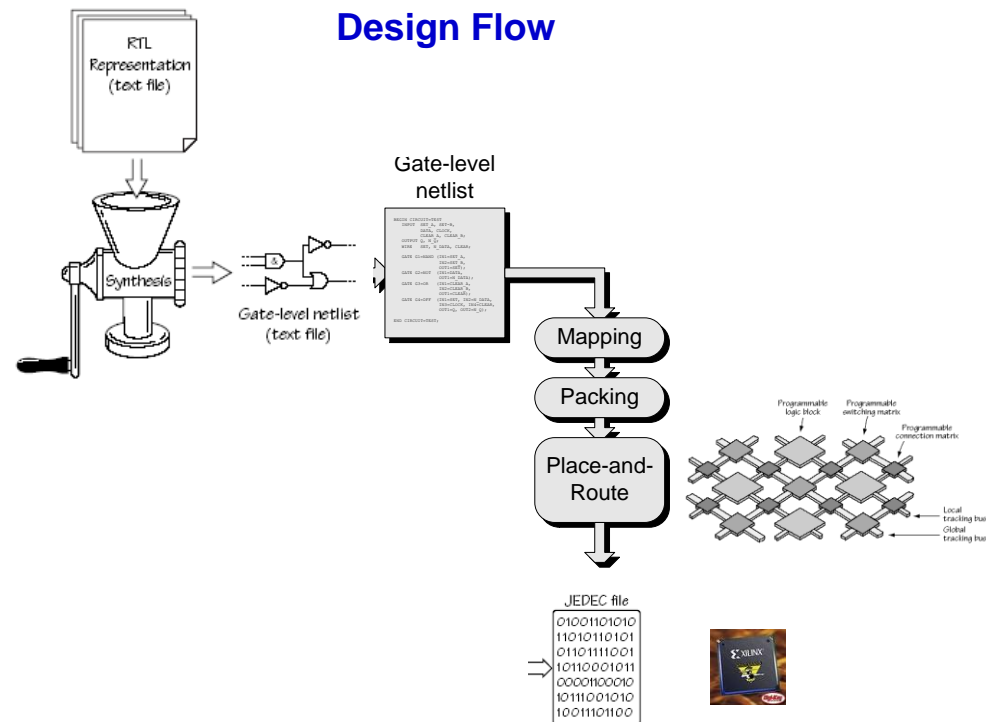
# FPGA EDA Tools

- High level Description of Logic Design
  - Hardware Description Language (Textual)
- Compile (Synthesise) into Netlist.
- Boolean Logic Gates.
- Target FPGA Fabric
  - Mapping
  - Routing
- Bit File for FPGA
- Commercial CAE Tools (Complex & Expensive)
- Logic Simulation



 
# FPGA Internals: Configurable Logic Blocks (CLBs)

- LUTs can only implement combinational logic
- Need flip-flops to implement sequential logic
- Add flip-flop to each LUT output
  - Configurable Logic Block (CLB)
    - LUT + flip-flops
  - Can program CLB outputs to come from flip-flops or from LUTs directly



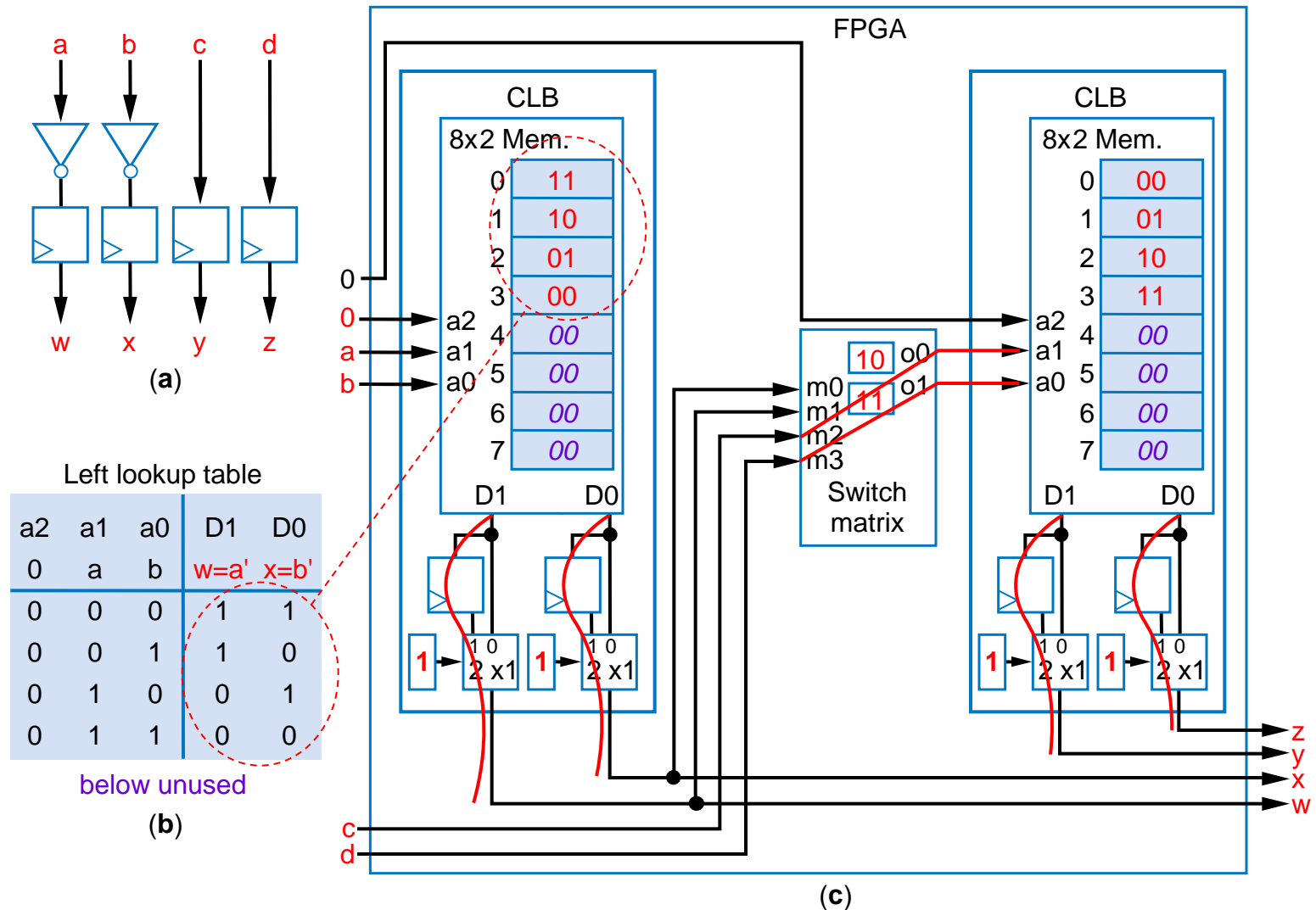
# FPGA Internals: Sequential Circuit Example using CLBs


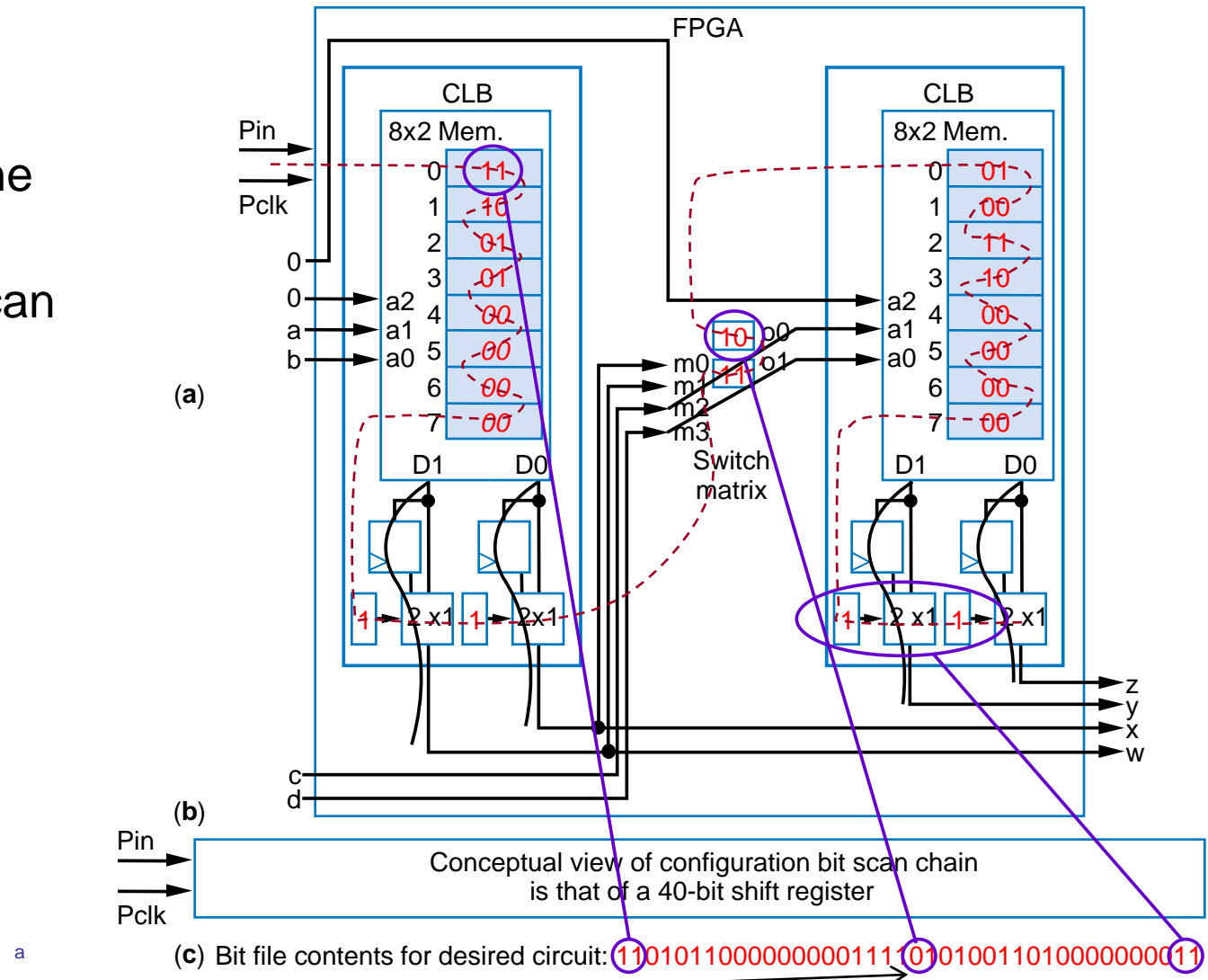
# FPGA Internals: Programming an FPGA


- All configuration memory bits are connected as one big shift register
  - Known as scan chain
- Shift in "bit file" of desired circuit



*This isn't wrong. Although the bits appear as "10" above, note that the scan chain passes through those bits from right to left – so "01" is correct here.*
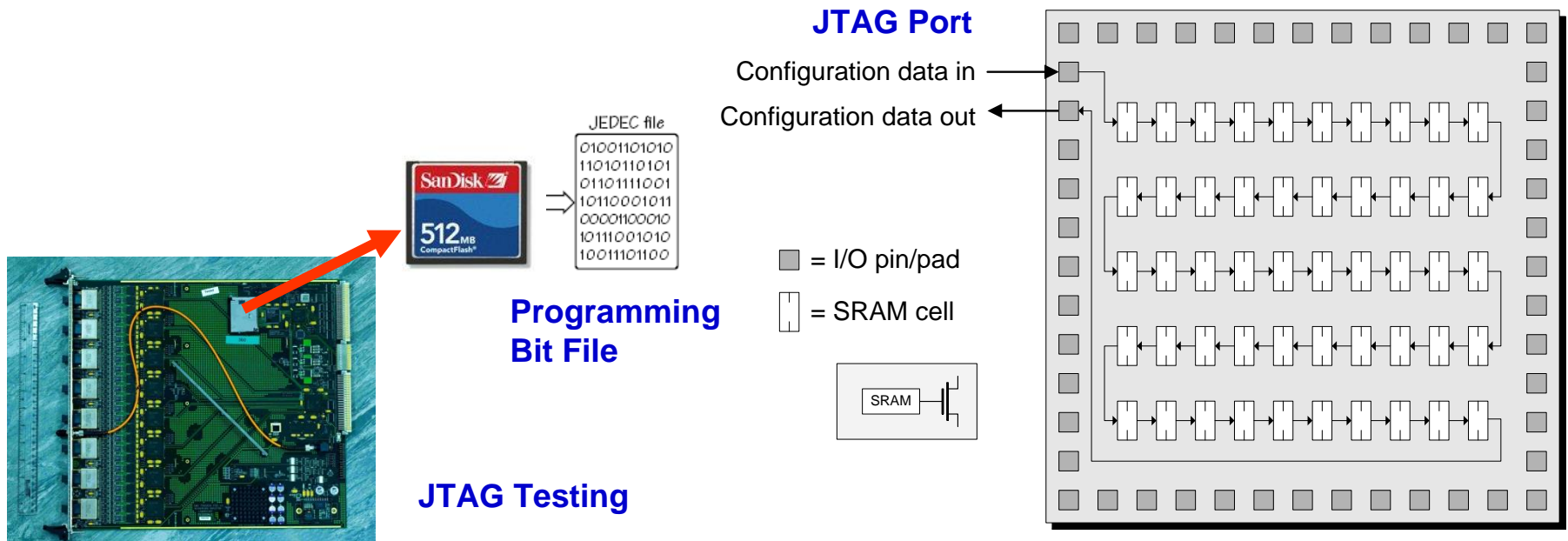
# Configuring an FPGA

- Millions of SRAM cells holding LUTs and Interconnect Routing
- Volatile Memory. Loses configuration when board power is turned off.
- Keep Bit Pattern describing the SRAM cells in non-Volatile Memory e.g. ROM or Digital Camera card
- Configuration takes ~ secs





# Summary

- Programmable Logic Devices
  - Basics
- Field Programmable Gate Arrays (FPGAs)
  - Architecture
- Design Flow
  - Hardware Description Languages
  - Design Tools

