 


Finite-State Machines **(FSMs) and Controllers**

More examples

- Complex counter
 - repeats 5 states in sequence
 - not a binary number representation
- Step 1: derive the state transition diagram
 - count sequence: 000, 010, 011, 101, 110
- Step 2: derive the state transition table from the state transition diagram



Present State			Next State			Flip flop input		
C	B	A	C'	B'	A'	D _C	D _B	D _A
0	0	0	0	1	0	0	1	0
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	1	0	1
1	0	1	1	1	0	1	1	0
1	1	0	0	0	0	0	0	0

counter example

Present State			Next State			Flip flop input		
C	B	A	C'	B'	A'	D _C	D _B	D _A
0	0	0	0	1	0	0	1	0
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	1	0	1
1	0	1	1	1	0	1	1	0
1	1	0	0	0	0	0	0	0

D_C

	C			
	0	0	0	X
A	X	1	X	1
	B			

D_B

	C			
	1	1	0	X
A	X	0	X	1
	B			


D_A

	C			
	0	1	0	X
A	X	1	X	0
	B			

$$D_C = A$$



$$D_B = B' + A'C'$$

$$D_A = BC'$$

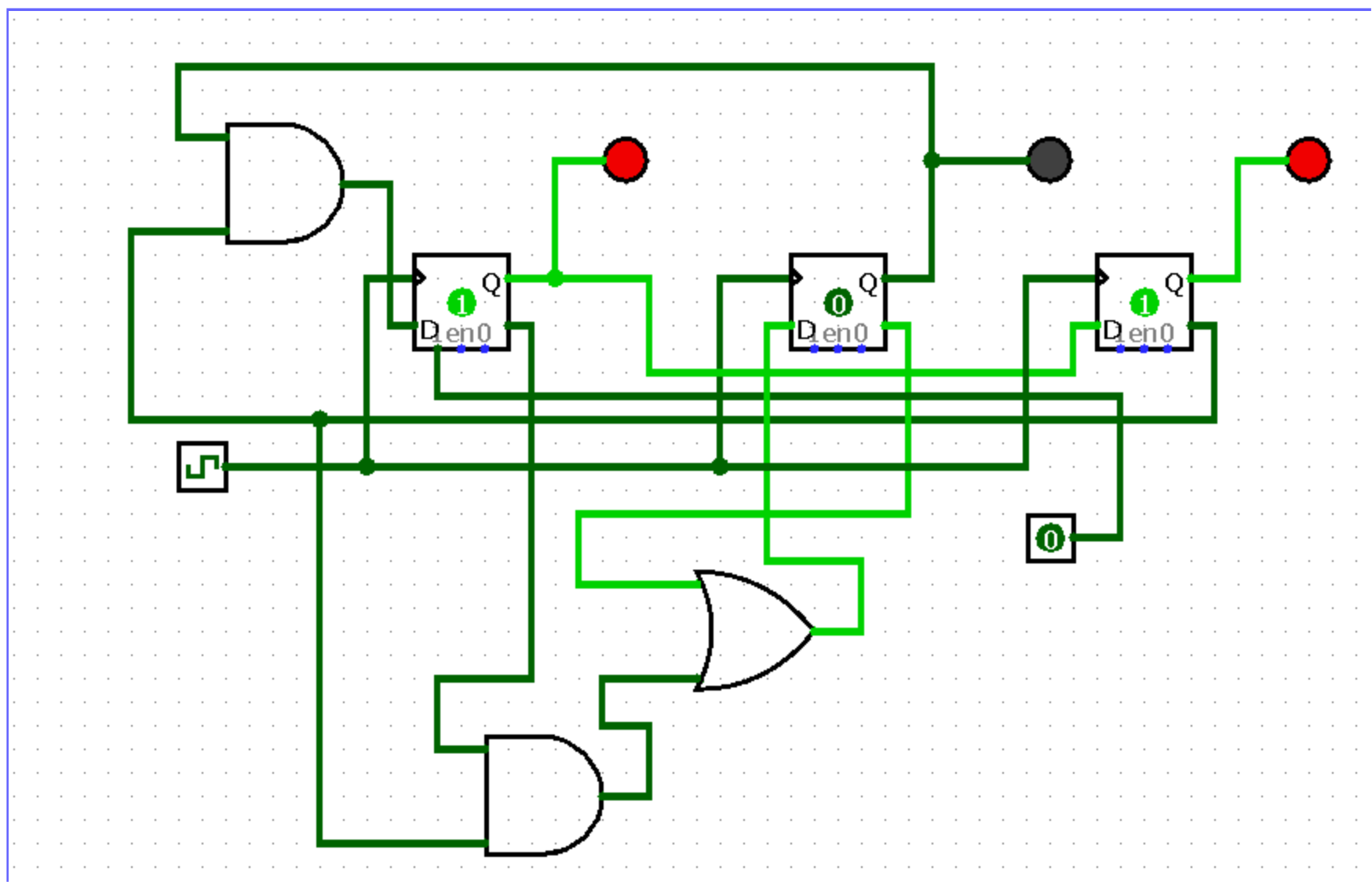

Self-starting counters

  - Start-up states
 - at power-up, counter may be in an unused or invalid state
 - designer must guarantee that it (eventually) enters a valid state
- Self-starting solution
 - design counter so that invalid states eventually transition to a valid state
 - may limit exploitation of don't cares



Self-starting counters

- Re-deriving state transition table from don't care assignment

$$D_C$$

	C			
	0	0	0	0
A	1	1	1	1
	B			


$$D_B$$

	C			
	1	1	0	1
A	1	0	0	1
	B			

$$D_A$$



	C			
	0	1	0	0
A	0	1	0	0
	B			

Present State			Next State		
C	B	A	C'	B'	A'
0	0	0	0	1	0
0	0	1	1	1	0
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	1	0	0

 


Finite-State Machines (FSMs) and Controllers

  - Want sequential circuit with particular behavior over time
- Example: Laser timer
 - Push button: $x=1$ for 3 clock cycles
 - How? Let's try three flip-flops
 - $b=1$ gets stored in first D flip-flop
 - Then 2nd flip-flop on next cycle, then 3rd flip-flop on next
 - OR the three flip-flop outputs, so x should be 1 for three cycles




Extend FSM to Three-Cycles High Laser Timer

 - Four states
- Wait in “Off” state while b is 0 (b')
- When b is 1 (and rising clock edge), transition to On1
 - Sets $x=1$
 - On next two clock edges, transition to On2, then On3, which also set $x=1$
- So $x=1$ for three cycles after button pressed





Standard Controller Architecture

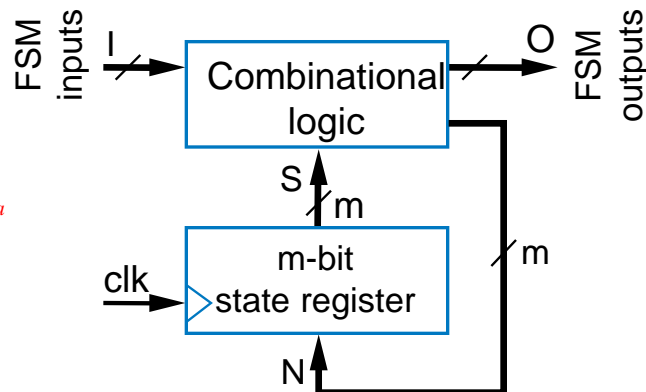- How implement FSM as sequential circuit?
 - Use standard architecture
 - State register -- to store the present state
 - Combinational logic -- to compute outputs, and next state
 - For laser timer FSM
 - 2-bit state register, can represent four states
 - Input b, output x
 - Known as **controller**



General version

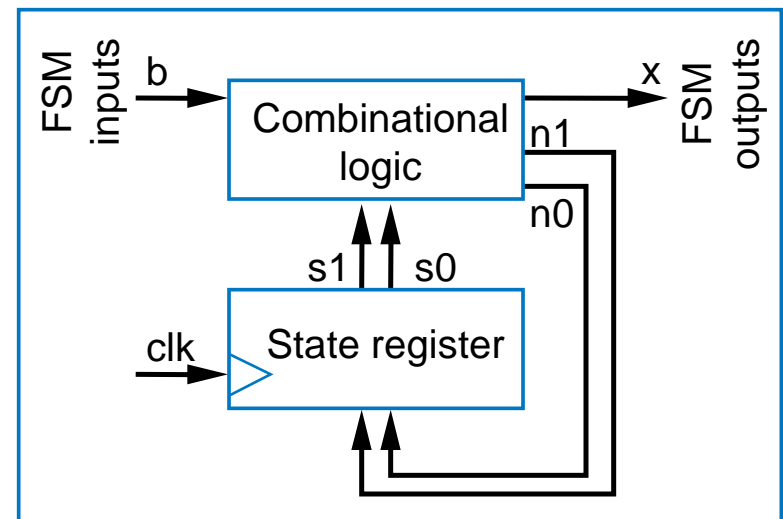 



Controller Design

- Five step controller design process

	Step	Description
Step 1	<i>Capture the FSM</i>	Create an FSM that describes the desired behavior of the controller.
Step 2	<i>Create the architecture</i>	Create the standard architecture by using a state register of appropriate width, and combinational logic with inputs being the state register bits and the FSM inputs and outputs being the next state bits and the FSM outputs.
Step 3	<i>Encode the states</i>	Assign a unique binary number to each state. Each binary number representing a state is known as an encoding . Any encoding will do as long as each state has a unique encoding.
Step 4	<i>Create the state table</i>	Create a truth table for the combinational logic such that the logic will generate the correct FSM outputs and next state signals. Ordering the inputs with state bits first makes this truth table describe the state behavior, so the table is a state table.
Step 5	<i>Implement the combinational logic</i>	Implement the combinational logic using any method.

Controller Design: Laser Timer Example

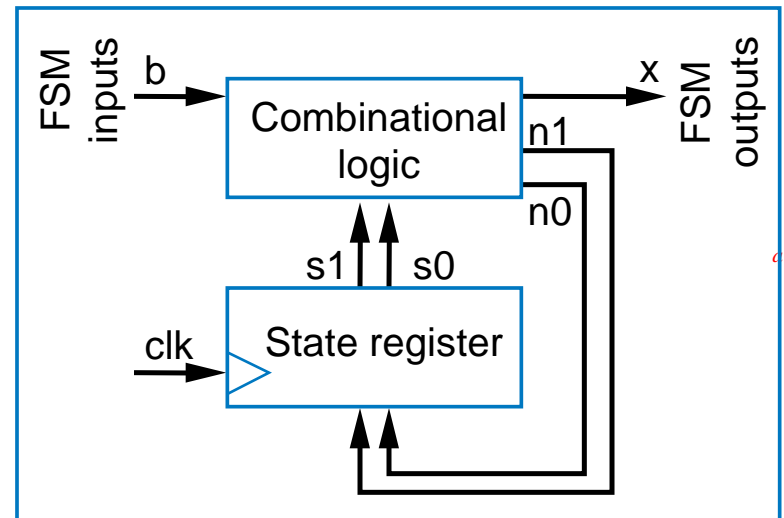 
- Step 1: Capture the FSM
 - Already done
- Step 2: Create architecture
 - 2-bit state register (for 4 states)
 - Input b, output x
 - Next state signals n1, n0
- Step 3: Encode the states
 - Any encoding with each state unique will work



Controller Design: Laser Timer Example (cont)

- Step 4: Create state table


	Inputs			Outputs		
	s1	s0	b	x	n1	n0
<i>Off</i>	0	0	0	0	0	0
	0	0	1	0	0	1
<i>On1</i>	0	1	0	1	1	0
	0	1	1	1	1	0
<i>On2</i>	1	0	0	1	1	1
	1	0	1	1	1	1
<i>On3</i>	1	1	0	1	0	0
	1	1	1	1	0	0

 

Controller Design: Laser Timer Example (cont)

- Step 5: Implement combinational logic

	Inputs			Outputs		
	s1	s0	b	x	n1	n0
<i>Off</i>	0	0	0	0	0	0
	0	0	1	0	0	1
<i>On1</i>	0	1	0	1	1	0
	0	1	1	1	1	0
<i>On2</i>	1	0	0	1	1	1
	1	0	1	1	1	1
<i>On3</i>	1	1	0	1	0	0
	1	1	1	1	0	0

 

$$x = s1 + s0 \text{ (note from the table that } x=1 \text{ if } s1 = 1 \text{ or } s0 = 1)$$

$$n1 = s1's0b' + s1's0b + s1s0'b' + s1s0'b$$

$$n1 = s1's0 + s1s0'$$

$$n0 = s1's0'b + s1s0'b' + s1s0'b$$

$$n0 = s1's0'b + s1s0'$$