
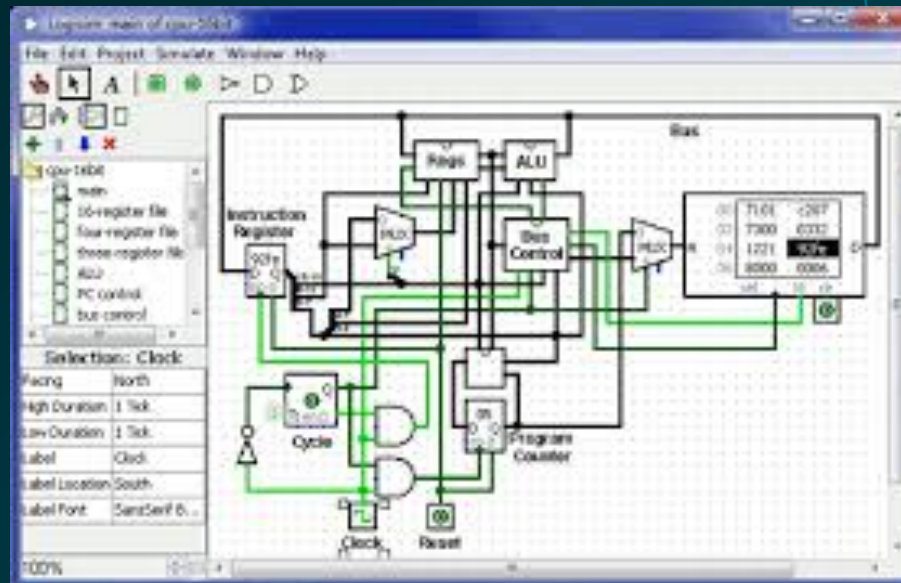
 


A series of thin, light blue geometric lines in the top right corner of the slide. These include a horizontal line, a vertical line, and several curved lines that intersect at a single point, creating a star-like or web-like pattern.


**CS225/CS226**

# So far

 

# Modern System

L2 Cache  
6MB  
L2 Cache  
6MB

 


Core 0


Core 1

Penryn (dual-core)  
45nm Technology

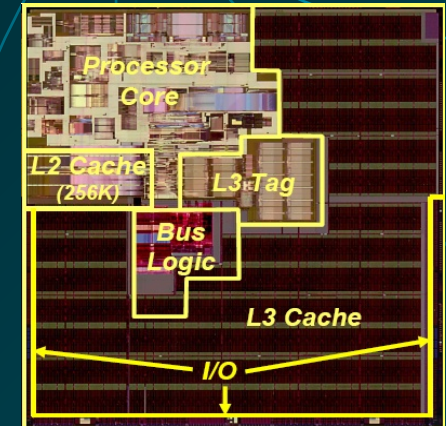Montecito\* (dual-core)  
(L2-24MB, L1-2MB)  
90nm Technology



Itanium 2\* (L3-9MB)  
130nm Technology

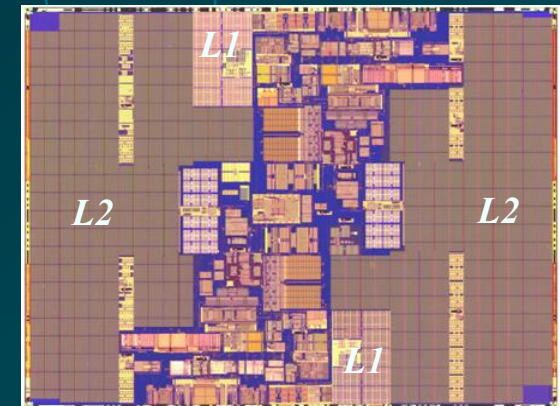



# *Different versions*



Silicon Process Technology

1.5 $\mu$

1.0 $\mu$

0.8 $\mu$

0.6 $\mu$

0.35 $\mu$

0.25 $\mu$

0.18 $\mu$

0.13 $\mu$

Intel386™ DX  
Processor




Intel486™ DX  
Processor




Pentium®  
Processor



 
Pentium®  
Pro  
Processor  
Pentium® II  
Processor




Pentium® III  
Processor

 

Pentium® 4  
Processor

 


# Basic Design Methodology

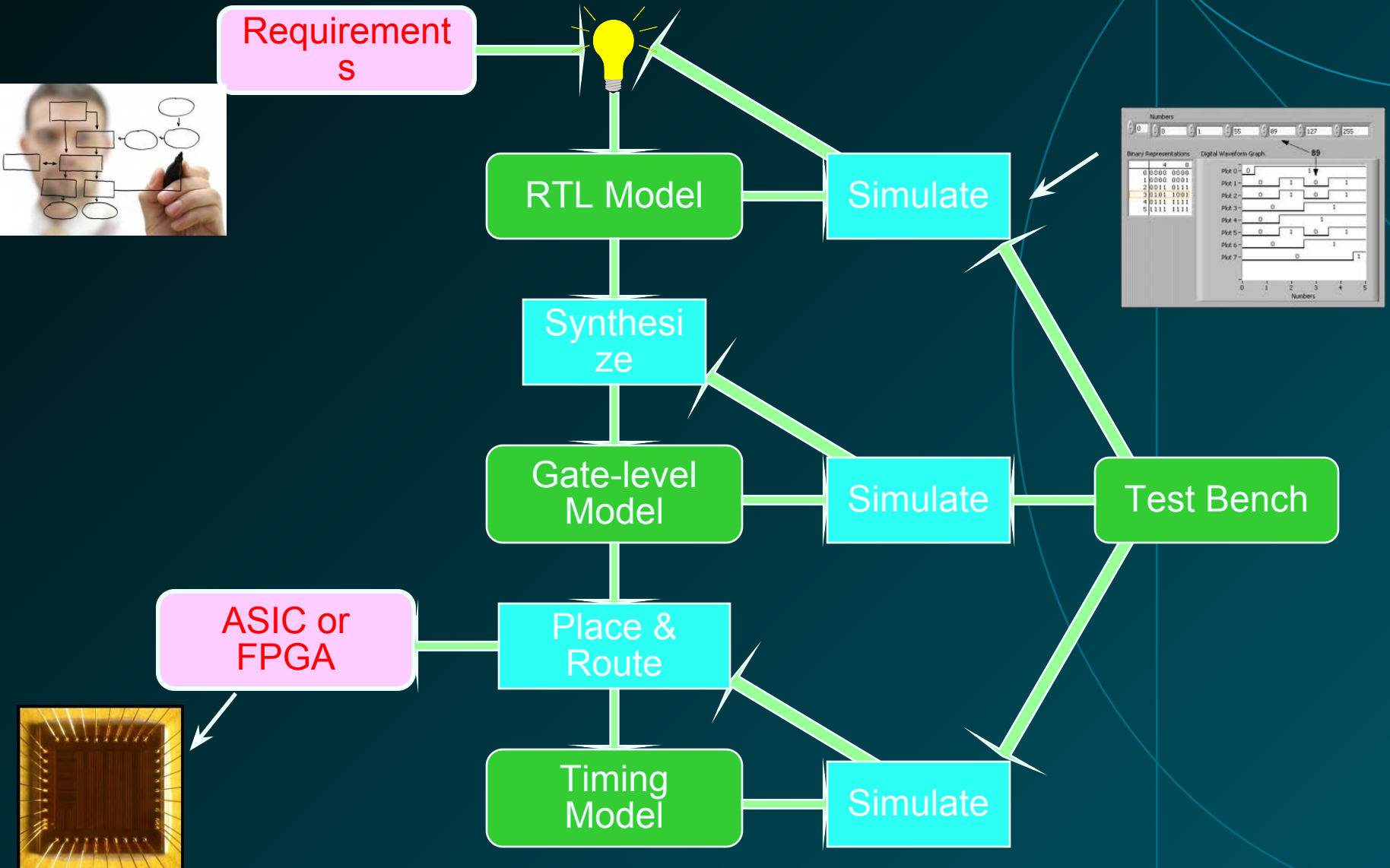

# Register Transfer Level (RTL) Design Description

Today's Topic

 


# Basic Design Methodology



Verilog

```
Always  
  inst1  
  inst2  
  inst3
```


Synthesis

 

mapping

  

Place and Route

 

# What is Verilog HDL?


- **Verilog Hardware Description Language(HDL)?**
  - **A high-level computer language can model, represent and simulate digital design**
    - Hardware concurrency
    - Parallel Activity Flow
    - Semantics for Signal Value and Time
  - **Design examples using Verilog HDL**
    - Intel Pentium, AMD K5, K6, Atheon, ARM7, etc
    - Thousands of ASIC designs using Verilog HDL


 
# VERILOG HDL

- Basic Unit – A module
- Module
  - Describes the functionality of the design
  - States the input and output ports
- Example:


```
module and_gate(out, a, b);  
output out ;  
input a, b;  
assign out = a & b;  
endmodule
```


 
# Testing AND gate

- Instantiate a module
  - apply test

```
module tb_and_gate();  
  reg a,b;  
  wire out;  
  and_gate uut (out,a,b); // this instantiates a and gate, uut is a label  
  initial  
  begin  
    a = 1'b0;           // here we apply inputs to the gate  
    b = 1'b0;  
    #10;  
    a = 1'b0;  
    b = 1'b1;  
    #10;  
    a = 1'b1;  
    b = 1'b1;  
    #10;  
    a = 1'b1;  
    b = 1'b0;  
    #10;  
  End  
endmodule
```




# Different Levels of Abstraction

- **Algorithmic**
  - the function of the system
- **RTL**
  - the data flow
  - the control signals
  - the storage element and clock
- **Gate**
  - gate-level net-list
- **Switch**
  - transistor-level net-list
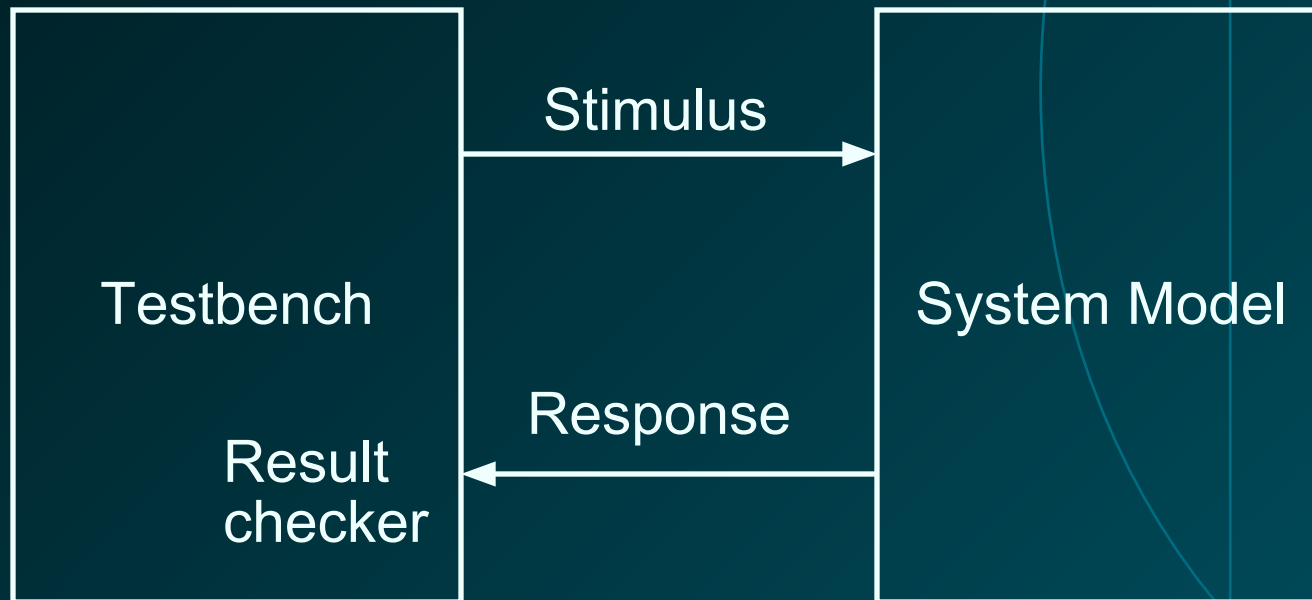
# How Are Simulators Used?

- Testbench generates stimulus and checks response
- Coupled to model of the system
- Pair is run simultaneously






# Sample Design

```
module fadder ( sum, cout, a, b , ci );  
// port declaration  
output sum, cout;  
input  a, b, ci;  
reg    sum, cout;  
// behavior description  
always @( a or b or ci )  
begin  
    sum = a ^ b ^ ci;  
    cout = ( a&b ) | ( b&ci ) | ( ci&a);  
end  
endmodule
```

## 1-bit full adder

 

# Writing Testbenches

```
module test;  
reg a, b, sel;
```

Inputs to device  
under test



```
mux m(y, a, b, sel);
```

Device under test



```
initial begin
```

\$monitor is a built-in  
event driven "printf"



```
    $monitor($time,, "a = %b b=%b sel=%b y=%b",  
              a, b, sel, y);
```

```
    a = 0; b= 0; sel = 0;
```

```
    #10 a = 1;
```

```
    #10 sel = 1;
```

```
    #10 b = 1;
```

```
end
```

Stimulus generated by  
sequence of  
assignments and delays




# Structural Modeling

- When Verilog was first developed (1984) most logic simulators operated on netlists
- Netlist: list of gates and how they're connected
- A natural representation of a digital logic circuit
- Not the most convenient way to express test benches
 
# Module basic\_gates

```
module basic_gates (x, y, z, f) ;  
input  x, y, z;  
output f ;  
wire a, b, c;  
// Structural modeling  
    nor g1 (b, x, y);  
    not  g2 (a, x);  
    and  g3 (c, a, z);  
    nor g4 (f, b, c);  
endmodule
```





# Behavioral Modeling

- A much easier way to write testbenches
- Also good for more abstract models of circuits
  - Easier to write
  - Simulates faster
- More flexible
- Provides sequencing
- Verilog succeeded in part because it allowed both the model and the testbench to be described together

# Two Main Components of Verilog

- **Concurrent, event-triggered processes (behavioral)**
  - *Initial* and *Always* blocks
  - can perform standard data manipulation tasks (assignment, if-then, case)
  - Processes run until they delay for a period of time or wait for a triggering event
- **Structure (Plumbing)**
  - Verilog program build from modules with I/O interfaces
  - Modules may contain instances of other modules
  - Modules contain local signals, etc.
  - Module configuration is static and all run concurrently

# Two Main Data Types

- **Nets represent connections between things**
  - Do not hold their value
  - Take their value from a driver such as a gate or other module
  - Cannot be assigned in an *initial* or *always* block
- **Regs represent data storage**
  - Behave exactly like memory in a computer
  - Hold their value until explicitly assigned in an *initial* or *always* block
  - Can be used to model latches, flip-flops, etc., but do not correspond exactly


# Description Styles

## ■ General definition

```
module module_name ( port_list );  
    port declarations;  
    ...  
    variable declaration;  
    ...  
    description of behavior  
endmodule
```
 
## □ Example

```
module HalfAdder (A, B, Sum Carry);  
input A, B;  
output Sum, Carry;  
assign Sum = A ^ B;  
// ^ denotes XOR  
assign Carry = A & B;  
// & denotes AND  
endmodule
```





# Description Styles (cont.)

```
module mux1( select, d, q );  
  input[1:0] select;  
  input[3:0] d;  
  output    q;  
  wire      q;  
  wire[1:0] select;  
  wire[3:0] d;  
  
  assign q = d[select];  
endmodule
```

# Description Styles (cont.)

- Behavioral: Algorithmically specify the behavior of the design

- Example:

```
always @( select or a or b ) begin
```

```
    if (select == 0) begin
```

```
        out = b;
```

```
    end
```

```
    else if (select == 1) begin
```

```
        out = a;
```

```
    end
```

```
end
```



# Description Styles (cont.)

```
module mux1( select, d, q );  
  input[1:0] select;  
  input[3:0] d;  
  output    q;  
  wire      q;  
  wire[1:0] select;  
  wire[3:0] d;  
  
  assign q = d[select];  
endmodule
```

# Description Styles (cont.)

```
module mux2( select, d, q );  
  input[1:0] select;  
  input[3:0] d;  
  output    q;  
  reg      q;  
  wire[1:0] select;  
  wire[3:0] d;  
  
  always @(d or select)  
    q = d[select];  
endmodule
```



# Description Styles (cont.)

```
module mux3( select, d, q );  
input[1:0] select;  
input[3:0] d;  
output q; reg q;  
wire[1:0] select;  
wire[3:0] d;  
always @( select or d ) begin  
    if( select == 0)  
        q = d[0];  
    if( select == 1)  
        q = d[1];  
    if( select == 2)  
        q = d[2];  
    if( select == 3)  
        q = d[3];  
end endmodule
```

# Description Styles (cont.)


```
module mux4( select, d, q );  
  input[1:0] select;  
  input[3:0] d;  
  output    q;  
  reg       q;  
  always @( select or d )  
  begin  
    case( select )  
      0 : q = d[0];  
      1 : q = d[1];  
      2 : q = d[2];  
      3 : q = d[3];  
    endcase  
  end  
endmodule
```

# Four-valued Data

- Verilog's nets and registers hold four-valued data
- 0, 1
  - Obvious
- Z
  - Output of an undriven tri-state driver
- X
  - Models when the simulator can't decide the value
  - Initial state of registers
  - When a wire is being driven to 0 and 1 simultaneously
 
# Four-valued Logic

- Logical operators work on three-valued logic



	0	1	X	Z
0	0	0	0	0
1	0	1	X	X
X	0	X	X	X
Z	0	X	X	X

← Output 0 if one input is 0

← Output X if both inputs are gibberish

# Nets and Registers

- Wires and registers can be bits, vectors, and arrays
- `wire b[3:0];`

`wire a;`                    **// Simple wire**

`reg [5:0] vec;`            **// Six-bit register**

`integer imem[0:1023];` **// Array of 1024 integers**

`reg [31:0] dcache[0:63];` **// A 32-bit memory**

`reg [31:0] regfile [0:63];` **// 64 registers each 32 bit**

# Modules and Instances

- Basic structure of a Verilog module:

```
module mymod(output1, output2, ... input1, input2);  
output output1;  
output [3:0] output2;  
input input1;  
input [2:0] input2;  
...  
endmodule
```

Verilog convention  
lists outputs first





# Instantiating a Module

- Instances of

```
module mymod(y, a, b);
```

- look like

```
mymod mm1(y1, a1, b1);    // Connect-by-position
```

```
mymod (y2, a1, b1),  
      (y3, a2, b2);
```

// Instance names omitted

```
mymod mm2(.a(a2), .b(b2), .y(y2)); // Connect-by-name
```

# Gate-level Primitives

- Verilog provides the following:

<b>and</b>	<b>nand</b>	<b>logical AND/NAND</b>
<b>or</b>	<b>nor</b>	<b>logical OR/NOR</b>
<b>xor</b>	<b>xnor</b>	<b>logical XOR/XNOR</b>
<b>buf</b>	<b>not</b>	<b>buffer/inverter</b>

- **Basic components for behavioral modeling**

- Runs when simulation starts
- Terminates when control reaches the end
- Good for providing stimulus

- Runs when simulation starts
- Restarts when control reaches the end
- Good for modeling/specifying hardware

[illegible]

# Initial and Always

- Run until they encounter a delay

initial begin

```
#10 a = 1; b = 0;
```

```
#10 a = 0; b = 1;
```

end

- or a wait for an event

always @(posedge clk)

```
q = d;
```

always

```
begin wait(i); a = 0;
```

```
wait(~i); a = 1;
```

end

# Binary Literals

- Valid digits: 0,1,z,Z,?,x,X  
(one bit per digit)
- Zero-filled to 32 bits
  - Filled with z or x if most significant bit
- Syntax 'b<digit> or 'B<digit>
- Example

'b0	0000 0000 ... 0000
'b1	0000 0000 ... 0001
'B1	0000 0000 ... 0001
'bx	xxxx xxxx ... xxxx
'b10x	0000 0000 ... 010x

# Decimal Literals

- Valid digits: 0, 1, ..9

(No X or Z)

- No bitwise correspondence
- Zero filled to 32 bits
- Syntax 'd<digit> or 'D<digit>
- Example

'd0                    0000 0000 ... 0000

'd1                    0000 0000 ... 0001

'D1 1                0000 0000 ... 1011



# Hexadecimal Literals

- Valid digits: 0-9, a-f, A-F, z, Z, ?, x, X
- Four bits per digit
- Zero filled to 32 bits
- Syntax 'h<digit> or 'H<digit>
- Example

'h0	0000 ...00000000
'h1	0000 ...00000001
'h1 1	0000 ...00010001
'hx	xxxx ...xxxxxxxxxx
'h17xz	000 ... 0010111xxxxzzzz

# Size of Literals

- By default 32 bit:
- Example

<code>'b0</code>	<code>0000 0000 ... 0000</code>
<code>'b1</code>	<code>0000 0000 ... 0001</code>
<code>'h1</code>	<code>0000 0000 ... 0001</code>
<code>'h0F</code>	<code>0000 0000 ... 1111</code>
<code>'d1</code>	<code>0000 0000 ... 0001</code>
<code>'d14</code>	<code>0000 0000 ... 1110</code>

# Sized Literals

- To specify number of bits different from 32
- For any literal base
- Extra bits are truncated
- example

1'b0	1
'b1	0000 0000 ... 0001
8'b1	0000 0001
8'h0F	00001111
8'd256	0000 0000
5'd14	01110

# Integer/Real Literals

- Valid digits: 0-9
- 2's compliment
- example

1            0000000 ... 0000000001

-1           11111111...111111111111

**35** 0000000 ... 0000100011

Real : Double precision (64 bits) floating point

Syntax: [-] <digit>.<digit> E[-] <digit>

example: 0.0

1.0

1.0E-9

# Logical Values

- Any non-zero value is **TRUE**
- Anything else is **FALSE**
  - Including 'x' and 'z'
- examples

1'b0	FALSE
1'b1	TRUE
1'bX	FALSE
3'b000	FALSE
3'b10X	TRUE
3'b00X	FALSE

# Operators

Arithmetic	Bitwise	Reduction	Relational
+: add -: subtract *: multiply /: divide %: modulus **: exponent	~: NOT &: AND  : OR ^: XOR ~^, ^~: XNOR	&: AND  : OR ~&: NAND ~ : NOR ^: XOR ~^, ^~: XNOR	>: greater than <: less than >=: greater than or equal <=: less than or equal
	case equality		Miscellaneous
Shift	===: equality !==: inequality	Logical	{ , }: concatenation {c{ }}: replication ?: conditional
<<: left shift >>: right shift <<<: arithmetic left shift >>>: arithmetic right shift	Equality ==: equality !=: inequality	&&: AND   : OR !: NOT	



# Bitwise Operators

- `~ <expr>`      *bitwise not*
- `<expr> & <expr>`      *bitwise and*
- `<expr> | <expr>`      *bitwise or*
- `<expr> ^ <expr>`      *bitwise xor*

- examples

<code>~3'b101</code>	<code>3'b010</code>
<code>3'b101 &amp; 3'b111</code>	<code>3'b101</code>
<code>3'b101   3'b111</code>	<code>3'b111</code>
<code>3'b101 ^ 3'b111</code>	<code>3'b010</code>

# Reduction Operators

- **&** <expr>      *and-* reduction
- **|** <expr>      *or-* reduction
- **^** <expr>      *xor-* reduction
- examples

<b>&amp;</b> 3'b011	1b0	<b> </b> 3'b011	1b1
<b>&amp;</b> 3'b111	1b1	<b> </b> 3'b000	1b0
<b>&amp;</b> 3'b11x	1bx	<b> </b> 3'b11x	1b1
<b>&amp;</b> 3'b01x	1b0	<b> </b> 3'b00x	1bx
	<b>^</b> 3'b001		1b1
	<b>^</b> 3'b111		1b1
	<b>^</b> 3'b11x		1bx

# Vector Operators

- `<expr> << <expr>`      *Logic shift left*
- `<expr> >> <expr>`      *Logic shift right*
- `{<expr> , <expr>}`      *Concatenation*
- `{<cont-expr>{expr}}`      *Replication*
- examples

<code>3'b101 &lt;&lt; 1</code>	<code>3'b010</code>
<code>3'b101 &gt;&gt; 2</code>	<code>3'b001</code>
<code>{3'b111, 1'b0}</code>	<code>4'b1110</code>
<code>{3 {2'b01}}</code>	<code>6'b010101</code>

# Relational Operators

- `<expr> == <expr>`      **equal**
- `<expr> != <expr>`      **not equal**
- `<expr> === <expr>`      ***identical***
- `<expr> !== <expr>`      ***not identical***

- **examples**

`3'b101 == 3'b010`      `'1b0 (False)`

`3'b101 != 3'b010`      `'1b1 (True)`

`3'b0x1 == 3'b0x1`      `'1b0 (False)`

`3'b0x1 === 3'b0x1`      `'1b1 (True)`

# Relational Operators

- `<expr> < <expr>`    *less than*
- `<expr> <= <expr>`    *less than or equal*
- `<expr> > <expr>`    *greater than*
- `<expr> != <expr>`    *greater than or equal*

- examples

`3'b101 < 3'b010`    `'1b0`

`3'b111 > 3'b010`    `'1b1`

`-1 < 1`    `'1b1`

# Logical Operators

- **!** <expr>            logical *not*
- <expr> **&&** <expr>    logical *and*
- <expr> **||** <expr>     logical *or*

- **examples**

**!** 3'b001            '1b0 (False)


3'b001 **&&** 3'b100        '1b1 (True)

3'b001 **&** 3'b100        '3b000 (False)

3'b001 **||** 3'b100        '1b1 (True)

# Combinational Circuit Design

- **Outputs are functions of inputs**

 

- **Examples**
  - MUX
  - decoder
  - priority encoder
  - adder



# Multiplexor

- Net-list (gate-level)

```
module mux2_1 (out,a,b,sel) ;
```

```
    output out ;
```

```
    input a,b,sel ;
```


```
    not (sel_, sel) ;
```

```
    and (a1, a, sel_) ;
```

```
    and (b1, b, sel) ;
```

```
    or (out, a1, b1) ;
```

```
endmodule
```

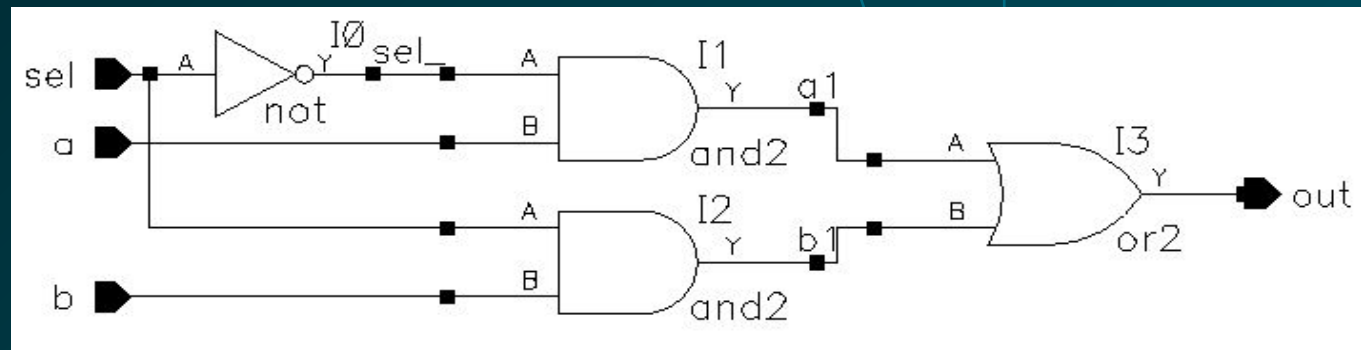

# Multiplexor

- **Continuous assignment**

```
module mux2_1 (out,a,b,sel) ;  
    output out ;  
    input a,b,sel ;  
    assign out = (a&~sel)|(b&sel) ;  
endmodule
```

- **RTL modeling**

```
always @(a or b or sel)  
if(sel)  
    out = b;  
else  
    out = a;
```

# Multiplexor

- 4-to-1 multiplexor


```
module mux4_1 (out, in0, in1, in2, in3, sel) ;  
    output out ;  
    input in0,in1,in2,in3 ;  
    input [1:0] sel ;  
    assign out = (sel == 2'b00) ? in0 :  
                (sel == 2'b01) ? in1 :  
                (sel == 2'b10) ? in2 :  
                (sel == 2'b11) ? in3 :  
                1'bx ;  
endmodule
```

# Multiplexor

```
module mux4_1 (out, in, sel) ;  
    output out ;  
    input [3:0] in ;  
    input [1:0] sel ;  
    reg out ;  
    always @(sel or in) begin  
        case(sel)  
            2'd0: out = in[0] ;  
            2'd1: out = in[1] ;  
            2'd2: out = in[2] ;  
            2'd3: out = in[3] ;  
            default: 1'bx ;  
        endcase  
    end  
endmodule
```
 
# Top-Down Design – Combinational Behavior to Structure Procedures with If-Else Statements

- **Q: Create procedure describing behavior of a 2x4 decoder using if-else-if construct**



2x4  
decoder

Order of assignment statements does not matter.

Placing two statements on one line does not matter.

To execute multiple statements if expression is true, enclose them between "begin" and "end"

```
`timescale 1 ns/1 ns

module Dcd2x4(I1, I0, D3, D2, D1, D0);

    input I1, I0;
    output D3, D2, D1, D0;

    reg D3, D2, D1, D0;

    always @(I1, I0)
    begin
        if (I1==0 && I0==0)
        begin
            D3 <= 0; D2 <= 0;
            D1 <= 0; D0 <= 1;
        end
        else if (I1==0 && I0==1)
        begin
            D3 <= 0; D2 <= 0;
            D1 <= 1; D0 <= 0;
        end
        else if (I1==1 && I0==0)
        begin
            D3 <= 0; D2 <= 1;
            D1 <= 0; D0 <= 0;
        end
        else
        begin
            D3 <= 1; D2 <= 0;
            D1 <= 0; D0 <= 0;
        end
    end
end
endmodule
```

# Decoder

- 3-to 8 decoder with an enable control

```
module decoder(o,enb_,sel) ;  
output [7:0] o ;  
input enb_ ;  
input [2:0] sel ;  
reg [7:0] o ;  
always @ (enb_ or sel)  
    if(enb_)  
        o = 8'b1111_1111 ;  
    else
```

```
        case(sel)  
            3'b000 : o = 8'b1111_1110 ;  
            3'b001 : o = 8'b1111_1101 ;  
            3'b010 : o = 8'b1111_1011 ;  
            3'b011 : o = 8'b1111_0111 ;  
            3'b100 : o = 8'b1110_1111 ;  
            3'b101 : o = 8'b1101_1111 ;  
            3'b110 : o = 8'b1011_1111 ;  
            3'b111 : o = 8'b0111_1111 ;  
            default : o = 8'bx ;  
        endcase  
    endmodule
```

# Priority Encoder

```
always @ (d0 or d1 or d2 or d3)
  if (d3 == 1)
```

```
    {x,y,v} = 3'b111 ;
```

```
  else if (d2 == 1)
```

```
    {x,y,v} = 3'b101 ;
```

```
  else if (d1 == 1)
```

```
    {x,y,v} = 3'b011 ;
```

```
  else if (d0 == 1)
```

```
    {x,y,v} = 3'b001 ;
```

```
  else
```

```
    {x,y,v} = 3'bxx0 ;
```

Inputs				Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$x$	$y$	$V$
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

# Parity Checker

```
module parity_chk(data,  
    parity);  
    input [0:7] data;  
    output parity;  
    reg parity;
```

```
    always @ (data)  
        begin: check_parity  
            reg partial;  
            integer n;  
            partial = data[0];  
            for ( n = 0; n <= 7; n = n + 1)  
                begin  
                    partial = partial ^ data[n];  
                end  
            parity = partial;  
        end  
    endmodule
```



# Left shift 2

```
module leftshift2_32(input  
    [31:0] a, output [31:0] y);
```

```
    assign y = {a[29:0], 2'b0};  
endmodule
```

```
module zeroext4_8(input [3:0] a,  
    output [7:0] y);
```

```
    assign y = {4'b0, a};
```

```
endmodule
```

# Test Bench

```
module testbench2(); reg a, b, c; wire y;
    example dut(a, b, c, y);
    // apply inputs one at a time; // checking results
    initial begin
        a = 0; b = 0; c = 0; #10;
        if (y !== 1) $display("000 failed.");
        c = 1; #10;
        if (y !== 0) $display("001 failed.");
        b = 1; c = 0; #10;
        if (y !== 0) $display("010 failed.");
        c = 1; #10;
        if (y !== 0) $display("011 failed.");
        a = 1; b = 0; c = 0; #10;
        if (y !== 1) $display("100 failed.");
        c = 1; #10;
        if (y !== 1) $display("101 failed.");
        b = 1; c = 0; #10;
        if (y !== 0) $display("110 failed.");
        c = 1; #10;
        if (y !== 0) $display("111 failed."); end
    endmodule
```

# Test Bench

```
module testbench3();  
    reg      clk, reset;  
    reg      a, b, c, yexpected;  
    wire     y;  
    reg [31:0] vectornum, errors;  
    reg [3:0] testvectors[10000:0];  
  
    // instantiate device under test  
    example dut(a, b, c, y);  
    // generate clock  
    always  
        begin  
            clk = 1; #5; clk = 0; #5;  
        end  
    // at start of test, load vectors // and pulse reset  
    initial  
        begin  
            $readmemb("example.tv", testvectors);  
            vectornum = 0; errors = 0;  
            reset = 1; #27; reset = 0;  
        end  
  
        // apply test vectors on rising edge of clk  
        always @(posedge clk)  
            begin  
                #1; {a, b, c, yexpected} = testvectors[vectornum];  
            end  
  
        // check results on falling edge of clk  
        always @(negedge clk)  
            if (~reset) begin // skip cycles during reset  
                if (y !== yexpected) begin // check result  
                    $display("Error: inputs = %b",  
                        {a, b, c});  
                    $display(" outputs = %b (%b expected)",  
                        y, yexpected);  
                    errors = errors + 1;  
                end  
                vectornum = vectornum + 1;  
                if (testvectors[vectornum] === 4'bx) begin  
                    $display("%d tests completed with %d errors",  
                        vectornum, errors);  
                    $finish;  
                end  
            end  
        end  
endmodule
```

# Test Bench



# Adder

- RTL modeling

```
module adder(c,s,a,b) ;  
  output c ;  
  output [7:0] s ;  
  input [7:0] a,b ;  
    assign {c,s} = a + b ;  
endmodule
```

- Logic synthesis

- CLA(carry look ahead) adder for speed optimization
- ripple adder for area optimization

# Tri-State

- The value z

**always @(sela or a)**  
**if (sela)**

out = a ;

**else**

out = 1'bz ;

- Another block


**always @(selb or b)**  
**if(selb)**

out = b ;

**else**

out = 1'bz ;

assign out = (sela)? a: 1'bz ;

 

# Keywords

**Note :** All keywords are defined in lower case

**Examples :**

module, endmodule

input, output, inout

reg, integer, real, time

not, and, nand, or, nor, xor

parameter

begin, end